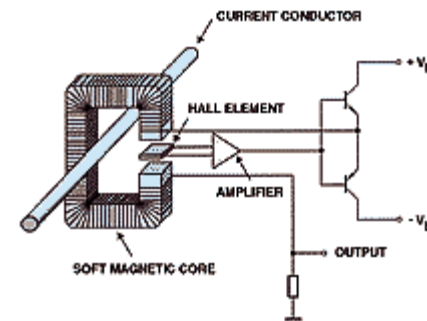


# Power and Energy Measurements

# Contest

- Power measurements
  - DC circuits
  - AC circuits
    - Three-phase systems
    - High-frequency power measurements
- Energy measurements
  - DC circuits
  - AC circuits
- Example: Power and energy measurements in motor drives




# Power in DC circuits


- Power
- Can be carried out using a voltmeter and an ammeter (generally)  
 $P = I_L V_L$
- Two measurement arrangements
- Wattmeter's:
  - Dynamometer
  - Digital wattmeter
  - Thermal wattmeter
  - Hall-power meter

# DC circuits

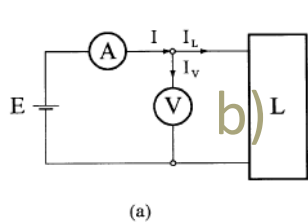- a) Ammeter measures current which flow into the voltmeter and load




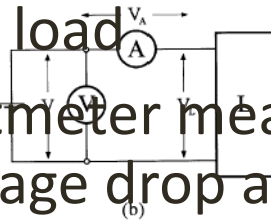b) Voltmeter measures voltage drop across the ammeter in addition to that dropping across the load


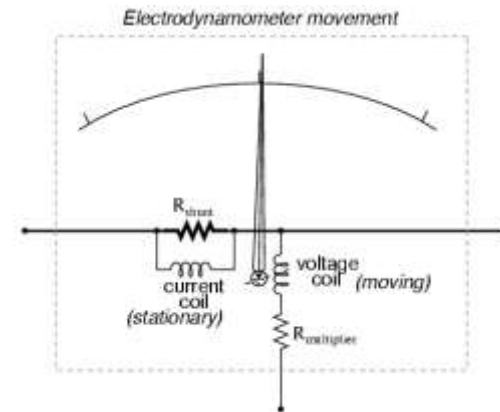
# Dynamometer

- Power (direct) measurement device for DC and AC systems
- Accuracy better than 0,25 %
- Two coils: static and movable
- Torque is proportional product of current in current coil and current in voltage coil



# Digital wattmeter (up to 100 kHz)

- Advantages:
  - High-resolution
  - Accuracy
- Several techniques (multiplication of signals)
- Electronic multiplier is an analog system which gives as its output a voltage proportional to the power indication required → A/D conversion





# Power in AC circuits

- Instantaneous power (time dependence)
- Mean power (usually the most interesting)
- Real power (active work), reactive power, apparent power
- Measures can be done same way as DC circuit (single-phase)

$$p(t) = v(t)i(t)$$

$$P = \frac{1}{T} \int_0^T p(t) dt$$

# AC circuits

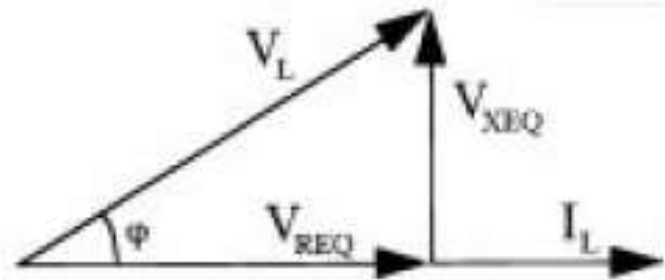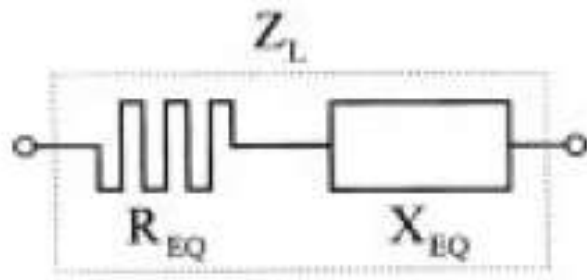


$$S = \sqrt{P^2 + Q^2}$$


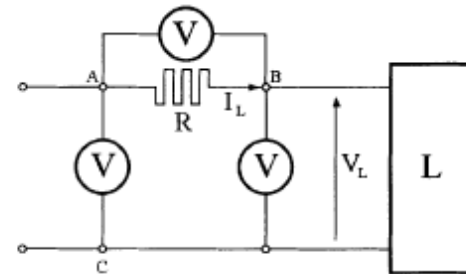
# Low- and Medium-Frequency Power Measurements

- Three-Voltmeter Method
  - Single-phase arrangements
  - Power in load can be measured using a non-inductive resistor and measuring the three voltage
  - Also in DC circuits

$$P_L = \frac{V_{AC}^2 - V_{AB}^2 - V_{BC}^2}{2R}$$



# Line-Frequency Power Measurements

- Polyphase Power Measurements
  - Three-phase systems are most commonly used in industrial applications
  - Energy and power generation and distribution
  - “Real power for consumer”
  - Reactive power also important (loading)
  - Power can measured several ways
  - Power factor

# Line-Frequency Power Measurements (2)

- Four (main) different cases which affects to the measurement arrangements:
  1. Symmetrical load with neutral conductor
  2. Symmetrical load without neutral conductor
  3. Unsymmetrical load with neutral conductor
  4. Unsymmetrical load without neutral conductor

# Line-Frequency Power Measurements (3)


- Measurements can be done several ways (needed arrangements):
  - One-wattmeter arrangements
  - Two-wattmeter arrangements
  - Three-wattmeter arrangements

# Symmetrical and Balanced systems

- The supply system is symmetrical and the three-phase load is balanced when phase currents and voltages are equal
- “Normal situation”

$$\begin{cases} V_1 = V_2 = V_3 \\ I_1 = I_2 = I_3 \end{cases}$$
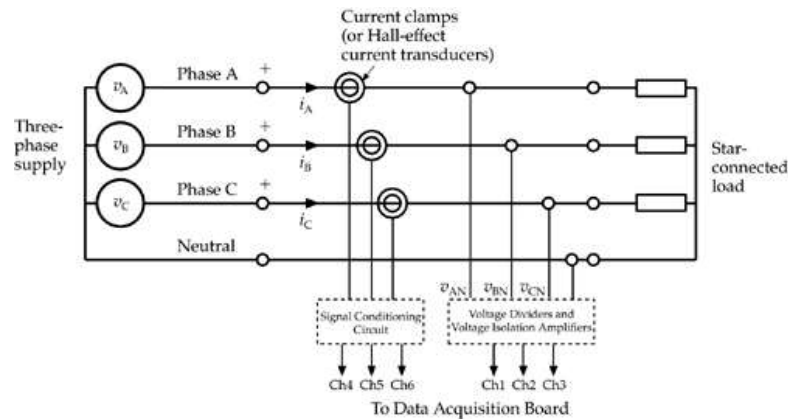
# Symmetrical load with neutral conductor




# Symmetrical load with neutral conductor (2)

- Number of wattmeters (voltage/current meter) is  $(n-1)$  where  $n$  is number of conductors
- If  $n=3$ , only one wattmeter are needed
- Power factor can be measured for example with “power factor meter”
- Powers:

$$\left\{ \begin{array}{l} S = V_1 I_1 + V_2 I_2 + V_3 I_3 \\ P = S \cos \delta \\ Q = S \sin \delta \end{array} \right.$$
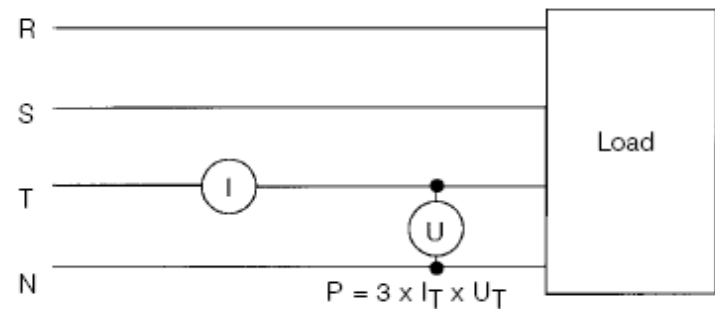
# Symmetrical load with neutral conductor (3)

- One wattmeter arrangements for real and reactive power measurements




$$P = 3U_T I_T \cos \delta$$


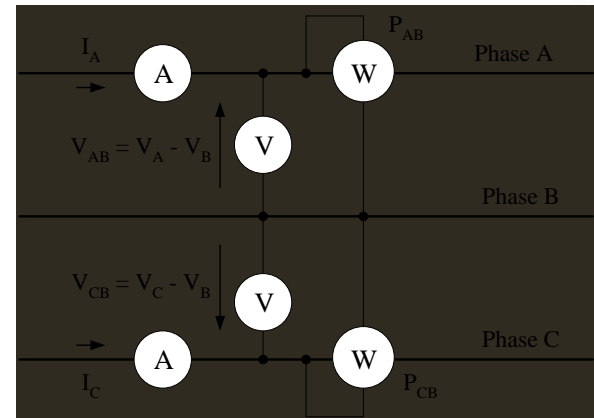
# Symmetrical load without neutral conductor

- Active and reactive power can be measured with two power meter (in three-wire system), case of symmetrical load and without neutral conductor (motors), Aron's theorem
- Possible to use also in case of unsymmetrical load
- If power factor is  $< 0,5$  then three wattmeter arrangement



$$P = P_{AB} + P_{CD}$$

$$Q = \sqrt{3} * (P_{AB} + P_{CD})$$

# Symmetrical Power Systems Supplying Unbalanced Loads


- Current amplitudes are different, and their relative phase is not equal  $120^\circ$
- Usually it is caused by some fault (short circuit)
- Three- or two wattmeter arrangements (depends on neutral point)

# Symmetrical Power Systems Supplying Unbalanced Loads

- Four possible arrangements:
  - Three-wattmeter arrangement
  - Two-wattmeter arrangement
  - Barbagelata arrangement
  - Righi arrangement
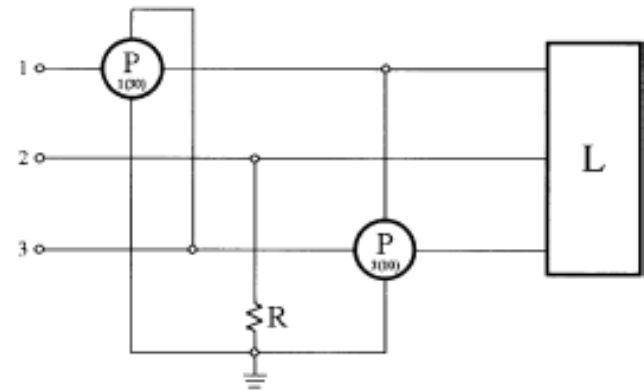
# Two-wattmeter arrangements

- Measurements arrangements for reactive power measurements




$$Q = \sqrt{3} \left[ -P_{1(30)} + P_{3(10)} \right]$$

- where  $P_{1(30)} = P_{10} - P_{13}$
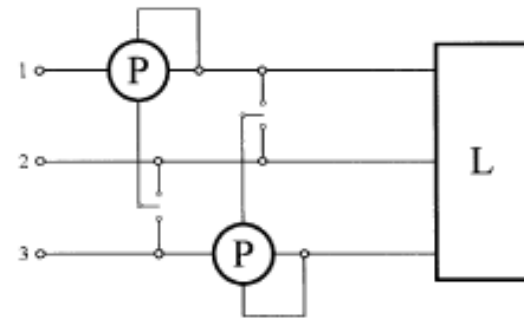
# Barbagelata arrangements


- Measurement arrangements for active and reactive power measurements
- “Two-wattmeter method”



$$\begin{cases} P = P_{12} + P_{32} \\ Q = \frac{1}{\sqrt{3}} [2(P_{13} - P_{31}) + P_{32} - P_{12}] \end{cases}$$

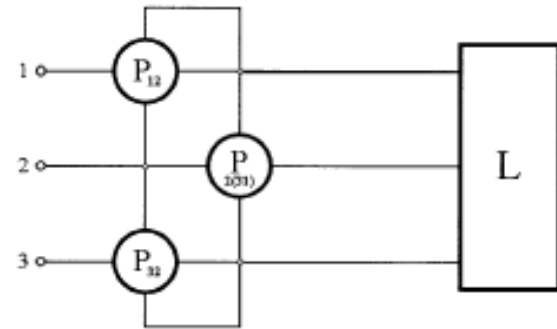
# Righi arrangements

- Measurement arrangements for reactive power measurements



$$Q = \frac{1}{\sqrt{3}} [P_{32} - P_{12} + 2P_{2(31)}]$$

# Conclusion about Three-Wire Systems

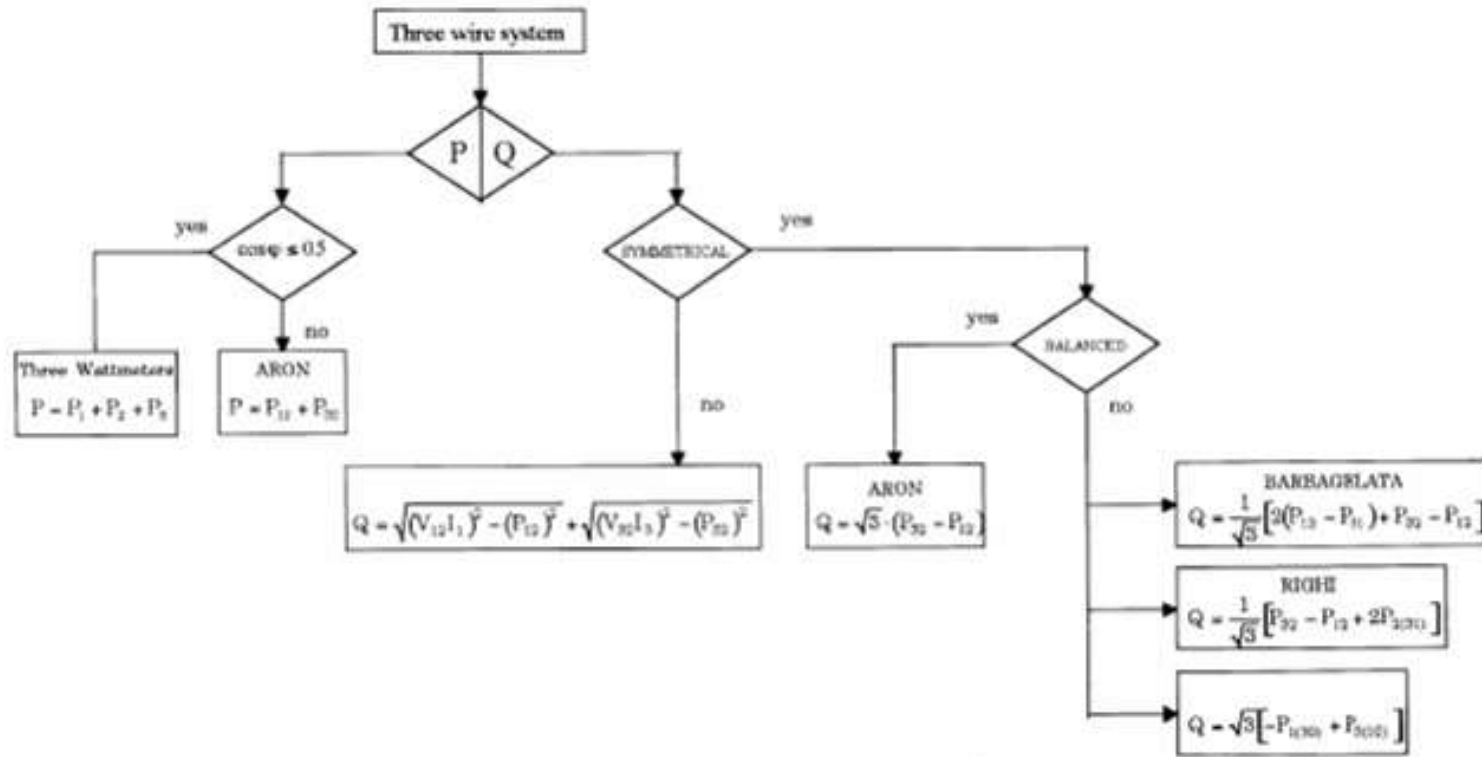

# High-frequency power measurements

- Radio (< 300 MHz) or microwave (> 1 GHz) frequencies
- Measurement devices are classified by absorption type and transmitted or throughline type
- Based on thermistors, thermocouples, diodes or radiation sensors
- Should be calibrated very carefully



# Energy measurements

- Simplest way is to measure current, voltage and observation interval and compute the product:

$$E = VI\Delta t = \int_{t_2}^{t_1} p(t)dt$$


- Observation interval measures by a chronometer or a time counter
- Electricity/energy meters:
  - Electrodynamic measurement device
  - Induction meter (AC)
  - Digital energy meter (AC/DC)
- Two main parts:
  - Transducer (Converts power to mechanical or electrical signal)
  - Counter (Integrates the “energy”)

# DC Energy Measurements

- Electrodynamic measurement device (integrating wattmeter)
- Based on DC motor (no iron)
- Magnetic field is generating by line current
- Torque


$$C_m = \frac{kIV}{R} = k_2 I_V \phi$$

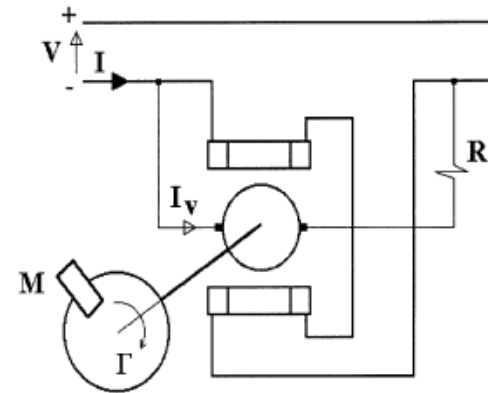- Aluminum disk and permanent magnet gives linear dependence of  $\Gamma$  and power
- Mechanical counter transfers the rotating motion into a digital or mechanical display



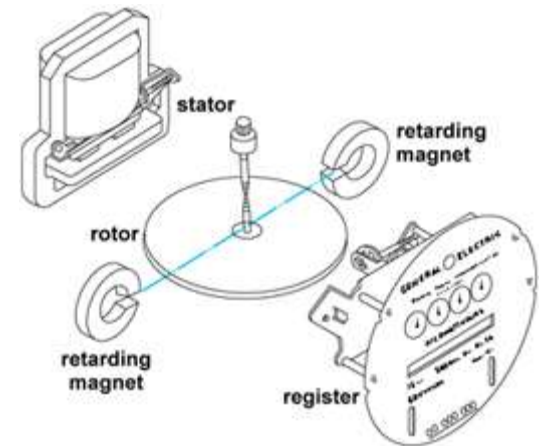
# AC Energy Measurements

- Induction energy meter (every household)
- Accuracy about 2 %
- Current and voltage coil
- AC current (coil) → Eddy currents (disk) → Force to disk
- Variable powers cause variable rotating speed
- Day and night electricity



# AC Energy measurements

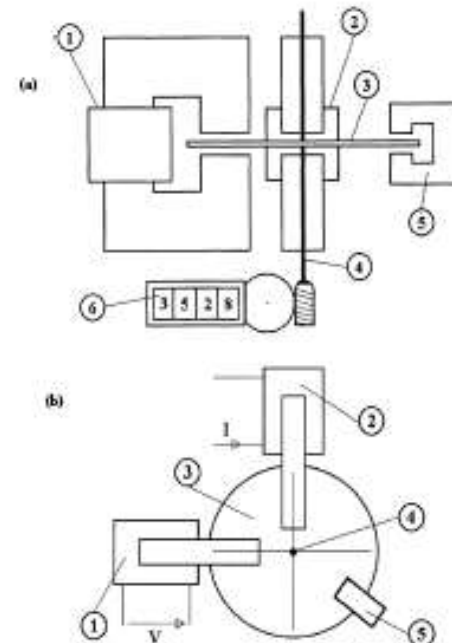1. Current coil and magnetic circuit
2. Voltage coil and magnetic circuit
3. Rotating disk
4. Disk axis
5. Permanent magnet
6. Display



# Energy measurements

- Automatic remote reading in future
  - Pricing
  - Controlling generation/loads
- Several system under development (GSM, radio link, phone line...)
- Energy meters also in var (reactive power) hours and volt-ampere (apparent power) hours

# The End

