 




## POWER ELECTRONICS



### NOTES

Course Instructor:

Associate Prof. Raza Jafri

Student:


TAIMUR MUSHARRAF  
05B-001-EE SEC:A

## Power Electronics :

(Combination of Power, Control & Electronics)

Defn:

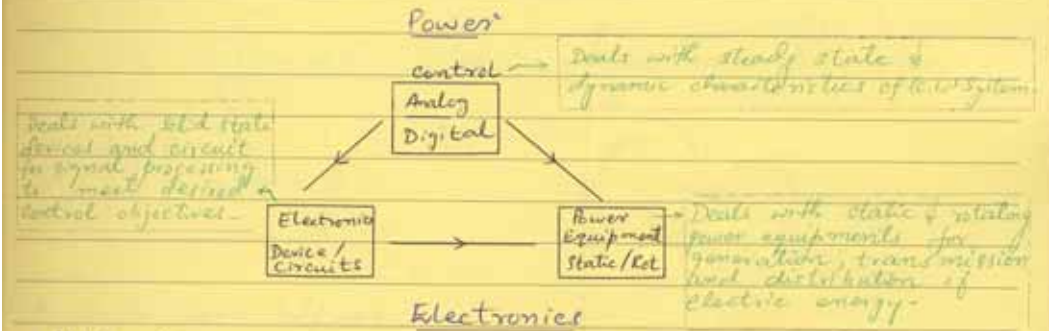"The applications of solid state electronics for the control & conversion of electrical power."



### Application:

- \* Heat Controls
- \* Light Controls
- \* Motor Controls
- \* Power Supplies
- \* Vehicle Propulsion Systems
- \* High Voltage Direct Current (HVDC)

Skin Effect: There is no skin effect w.r.t D.C.

\* Skin effect based on the frequency of A.C. we caused  $X_c \neq X_L$  (Losses).

In a conductor carrying an alternating current, an electromagnetic effect which results in current density being greater at surface of conductor than in centre. At sufficiently high frequencies current is practically confined to surface of conductor.

# Ac to Dc Conversion

Date 07-02-2009

(2)

## UNCONTROLLED RECTIFICATION






Rectifier: Converts AC to DC.

Depending upon i/p supply there are two types of rectification:

- (i) Single Phase
- (ii) Three Phase

(For simplification in analysis considering diodes to be lossless or ideal - meaning no forward voltage drop)

## SINGLE PHASE HALF-WAVE RECTIFIER

     


(Fig-3.1)

A Single Phase half wave rectifier is the simplest power electronics based circuit that is used only rarely for low cost power supplies that are used in radios.

The o/p is discontinuous and contains harmonics we expect from rectifier to have constant dc o/p with minimal harmonics.

For i/p side it must have a high power (ideally units) that means i/p current and voltage must be in phase.

 

Date 07-02-08

(3)

- \* Discontinuous nature of wave  $\Rightarrow$  Harmonic Distortion.
- \* As # of harmonics increases its strength decreases. Harmonics are the integral multiple of fundamental.

## PERFORMANCE PARAMETERS:

- Power factor is defined as  $P = VI$  (DC)
- $P = VI \cos \phi$  (AC)
- The average value of o/p load voltage,  $V_{dc}$
- " " " " " current,  $I_{dc}$
- Output dc Power is given as:  
 $P_{dc} = V_{dc} \cdot I_{dc}$  (3.1)
- The root-mean-square (rms) value of o/p voltage,  $V_{rms}$
- " " " " " Current,  $I_{rms}$
- Output ac Power is:  
 $P_{ac} = V_{rms} \cdot I_{rms}$  (3.2)
- The  $\eta$  (efficiency) or rectification ratio, w/c is a figure of merit and permit us to compare effectiveness, is defined as  
 $\eta = \frac{P_{dc}}{P_{ac}}$  (3.3)
- The o/p voltage can be considered as compound of two components:
  - (1) The DC value
  - (2) The AC component or ripple.

- The effective rms value of the ac component of output voltage is

$$V_{ac} = \sqrt{V_{rms}^2 - V_{dc}^2} \quad (3.4)$$

- The form factor, which is measure of shape of output voltage is

$$FF = \frac{V_{rms}}{V_{dc}} \quad (3.5)$$

- The ripple factor, which is measure of ripple content, is defined as

$$RF = \frac{V_{ac}}{V_{dc}} \quad (3.6)$$

Substituting Eq (3.4) in (3.6) the ripple factor can be expressed as


$$RF = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1} = \sqrt{FF^2 - 1} \quad (3.7)$$

- The transformer utilization factor is defined as

$$TUF = \frac{P_{dc}}{V_s I_s} \quad \text{* released is not written due to lenitive leach.} \quad (3.8)$$

where  $V_s$  &  $I_s$  are the rms voltage and current of transformer secondary respectively.

Let us consider waveform of fig 3.2 where  $V_s$  is sinusoidal i/p voltage and  $I_s$  is the sinusoidal i/p current and  $i_o$  is fundamental component.

 

(Fig 3.2)

- If  $\phi$  is angle b/w fundamental components of i/p current and voltage,  $\phi$  is called Displacement factor and defined as

$$DF = \cos \phi \quad (3.9)$$

- The Harmonic factor of input current is given as

$$HF = \left(\frac{I_s^2 - I_{s1}^2}{I_{s1}^2}\right)^{1/2} = \left[\left(\frac{I_s}{I_{s1}}\right) - 1\right]^{1/2} \quad (3.10)$$

where  $I_{s1}$  is fundamental comp. of i/p current  $I_s$ . Both  $I_s$  and  $I_{s1}$  are rms here.

- The input Power factor is defined as

$$PF = \frac{V_s I_{s1} \cos \phi}{V_s I_s} = \frac{I_{s1} \cos \phi}{I_s} \quad (3.11)$$

- The Crest factor which is measure of Peak i/p current  $I_s(\text{peak})$  as compared with its rms value  $I_s$ , is often of interest to specify peak current rating of devices and components. CF of i/p current is defined as

$$CF = \frac{I_s(\text{peak})}{I_s} \quad (3.12)$$

#### NOTES:

- HF is measure of distortion of a waveform and is also known as Total Harmonic Distortion (THD).
- If i/p current  $I_s$  is purely sine,  $I_{s1} = I_s$  &  $PF = DF$ . The  $\phi$  becomes impedance angle  $\theta = \tan^{-1}(wL/R)$  for RL load.
- DF is often known as Displacement Power factor (DPF)
- An ideal rectifier should have  $\eta = 100\%$ ,  $V_{ac} = 0$ ,  $RF = 0$ ,  $TUF = 1$ ,  $HF = THD = 0$ ,  $PF = DPF = 1$ .


(Example 3.1)

Date 07-02-08

Question No.1: Find performance parameter of Half wave rectifier. The rectifier in fig 3.1a has a purely resistive load of resistor (R). Determine

- (a) Efficiency (b) FF (c) RF (d) TUF (e) PIV of  $D_1$
- (f) CF of  $V_p$  Current (g)  $V_p$  PF.

Solution:

 

The average d/p voltage  $V_{dc}$  is defined as,

$$V_{dc} = \frac{1}{T} \int_0^T v_L(t) dt$$

We can notice from fig no.3.1 (b), the  $v_L(t) = 0$  for  $T/2 \leq t \leq T$ . Hence we have

$$\begin{aligned}
 V_{dc} &= \frac{1}{T} \int_0^{T/2} V_m \sin wt dt \\
 &= \frac{V_m}{T} \left[ -\frac{\cos wt}{\omega} \right]_0^{T/2} \\
 &= -\frac{V_m}{\omega T} \left\{ \cos \frac{\omega T}{2} - \cos 0 \right\} \\
 &= -\frac{V_m}{\omega T} \left\{ \cos \omega T - 1 \right\}
 \end{aligned}$$

$$\begin{aligned}
 V_{dc} &= \frac{-V_m}{2\pi \times \frac{1}{2}} \left\{ \cos 2\pi \times \frac{1}{2} - 1 \right\} \\
 V_{dc} &= \frac{-V_m (-2)}{2\pi} = \frac{V_m}{\pi}
 \end{aligned}$$

However freq of source is  $f = \frac{1}{T}$  &  $\omega = 2\pi f$

Thus,  $V_{dc} = \frac{V_m}{\pi} = 0.318 V_m$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{0.318 V_m}{R}$$

The rms value of periodic waveform is defined as

$$V_{rms} = \left[ \frac{1}{T} \int_0^T v_L^2(t) dt \right]^{1/2}$$

Date

$$\begin{aligned}
 V_{rms} &= \left[ \frac{1}{T} \int_0^{T/2} (V_m \sin wt)^2 dt \right]^{1/2} \\
 &= \frac{V_m}{2} = 0.5 V_m
 \end{aligned}$$

$$I_{rms} = \frac{V_{rms}}{R} = \frac{0.5 V_m}{R}$$

(a)

$$\begin{aligned}
 \eta &= \frac{P_{dc}}{P_{ac}} = \frac{(0.318 V_m) \left( \frac{0.318 V_m}{R} \right)}{(0.5 V_m) \left( \frac{0.5 V_m}{R} \right)} \\
 &= 0.4044 \times 100 \\
 \eta &= 40.44 \%
 \end{aligned}$$

(b)

$$\begin{aligned}
 FF &= \frac{V_{rms}}{V_{dc}} \\
 &= \frac{0.5 V_m}{0.318 V_m} \\
 &= 1.572 \quad \text{or} \quad 157.2 \%
 \end{aligned}$$

(c)

$$\begin{aligned}
 RF &= \frac{V_{ac}}{V_{dc}} \\
 RF &= \sqrt{FF^2 - 1} \\
 RF &= \sqrt{(1.57)^2 - 1} = 1.21 \quad \text{or} \quad 121 \%
 \end{aligned}$$

(d)

$$\begin{aligned}
 TUF &= \frac{V_s}{V_o} \\
 V_s &= \frac{V_m}{\sqrt{2}} = 0.707 V_m \\
 TUF &= \frac{P_{dc}}{V_s I_s}
 \end{aligned}$$

$$I_s = \frac{0.5 V_m}{R}$$

$$\text{New TUF} = \frac{0.318 V_m \times 0.318 \frac{V_m}{R}}{0.707 V_m \times 0.5 \frac{V_m}{R}}$$

$$\text{TUF} = 0.286$$

$$(f) \text{PIV} = V_m \quad \frac{1}{\text{TUF}} = 3.496$$

$$I_s(\text{peak}) = \frac{V_m}{R}, \quad I_s = \frac{0.5 V_m}{R}$$

$$\text{CF} = \frac{I_s(\text{peak})}{I_s}$$

$$\text{CF} = \frac{1}{0.5} = 2$$

$$(g) \text{I/p PF} = \frac{P_{ac}}{VA} = \frac{(0.5)^2}{0.707 \times 0.5} = 0.707$$

Notes:  $1/\text{TUF} = 3.496$  signifies that  $t_{xfr}$  must be 3.496 times larger than when it is used to deliver power from a pure ac voltage. This rectifier has ripple factor of 121% ; a low efficiency 40.5% and poor TUF 0.286. In addition  $t_{xfr}$  has to carry a dc current and this results in a dc saturation problem of transformer core.


\* TUF  $\rightarrow$  How lossy is system? more losses less the TUF. (Transformer Utilization Factor).

Core Saturation:



Single Phase Half Wave Rectifier with RL Load

 \* Due to inductive load conduction period of diode will extend beyond  $180^\circ$  until current becomes zero at  $\omega t = \pi + \delta$





\* The average o/p voltage is given by:

$$V_{dc} = \frac{V_m}{2\pi} \int_{\pi}^{\pi+\delta} \sin \omega t d(\omega t) = \frac{V_m}{2\pi} [-\cos \omega t]_{\pi}^{\pi+\delta}$$

$$V_{dc} = \frac{V_m}{2\pi} [1 - \cos(\pi + \delta)]$$

$$I_{dc} = \frac{V_{dc}}{R}$$

  

Free wheeling Concept:

\* The average  $V$  and  $I$  can be inc $\uparrow$  by making  $\delta = 0$  w/c is possible by adding FREE WHEELING Diode(s).

\* The fms of diode is that restricts -ve voltage developing across load. This inc $\uparrow$  magnets stored energy of inductor.

\* At  $t_1 = \pi/\omega$  current is transferred from  $D_1$  to  $D_m$  & process is called diode commutation. The waveforms are:



\* If 'L' value is inc $\uparrow$  so that waveform will be comes continuous




- \* Depending upon load time constant current can be continuous or discontinuous.
- \* Its discontinuous with a R-load & continuous with a highly inductive load.
- \* The continuity of highly current would depend upon time constant w/c is given by

$$\tau = \frac{WL}{R}$$

  
Single Phase Full-wave Rectifier with a Resistive load



 \* In this design PIV max of diode is to be chosen high limit or rating.



\* The average o/p voltage is given by:

 


$$V_{dc} = \frac{2}{\pi} \int_0^{\pi/2} V_m \sin wt dt$$

$$V_{dc} = \frac{2}{\pi} V_m = 0.6366 V_m \quad (3.21)$$


(Fig. 3.5)

\* Instead of using Center tapped txf, we can use 4 diode bridge rectifier circuit as shown:

Date 14-02-2008

 

(Fig 3.6)

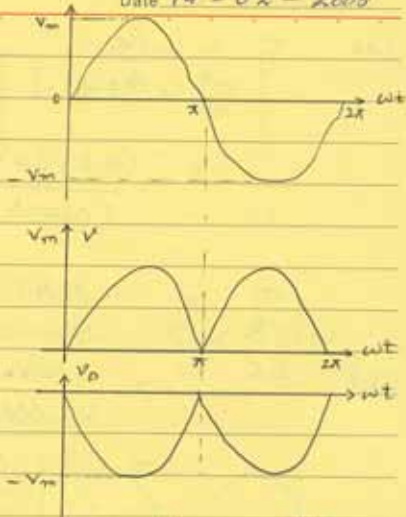

Example: 3.4 Finding Performance Parameters of a full-wave rectifier with center-tapped transformer.

If rectifier in Fig 3.5 has purely resistive load of R, determine (a) efficiency (b) PF (c) RF (d) TUF (e) PIV of Di and (f) CF of Ip current.

Solution:

$$V_{dc} = \frac{2V_m}{\pi} = 0.6366 V_m$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{0.6366 V_m}{R}$$

$$V_{rms} = \left[ \frac{2}{T} \int_0^{T/2} (V_m \sin \omega t)^2 dt \right]^{1/2} = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

$$I_{rms} = \frac{V_{rms}}{R} = \frac{0.707 V_m}{R}$$

Date

(a)  $\eta = \frac{P_{dc}}{P_{ac}}$

$$= \frac{(0.6366 V_m) (0.6366 \frac{V_m}{R})}{(0.707 V_m) (0.707 \frac{V_m}{R})}$$

$$\eta = 0.81 = 81\%$$

(b)  $PF = \frac{V_{rms} I_{dc}}{V_{dc} I_{rms}}$

$$= \frac{0.707 V_m}{0.6366}$$

$$= 1.1105 \text{ or } 111\%$$

(c)  $RF = \frac{V_{ac}}{V_{dc}}$

$$= \frac{1}{\sqrt{(1.1105)^2 - 1}}$$

$$RF = 0.483 \quad 48.3\%$$

(d) TUF

$$V_s = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

$$I_s = \frac{0.5 V_m}{R}$$

$$TUF = \frac{P_{dc}}{2 V_s I_s}$$

$$= \frac{1}{1.41} = 0.57$$

Date 14-02-2008

(e)  $PIV = -2V_m$

(f)  $CF = \frac{I_s(peak)}{I_s}$


$CF = 2$

$I_s(peak) = \frac{V_m}{R}$


Ans

### Single Phase Full-wave Rectifier

with R-L Load.

 

(a)

 


(b)

\* Construction of Inverter this phenomenon is very useful to introduce an inductor. Because for pure sine-wave  $\omega L$  makes it.



Supply line current

 

(d) Discontinuous Current.

\* L is used where minute timing is needed.

Date 14-02-2008

\* Two way controlling  $I_o$  or  $i_o$  current can be changed continuously or discontinuous depends upon value of these elements.  
\* And gap  $\beta$  to  $\alpha$  will be filled by inductance variation.


Q: Consider a full wave rectifier that has been designed to supply  $I_{dc} = 1A$  at 12 VDC compare the two possible designs for the implementation of set rectifier & compute the values of various performance parameters. Discuss the effect of increasing or dec + the Firing angle ' $\theta$ ' if diodes w/c were are using are controllable devices.  
(Next week : before Wednesday class)



## INTRODUCTION TO UNCONTROLLED 3 PHASE Rectification

\* The 3 phase system provides good efficiency means optimal level of performance.

(Fig 3.13)

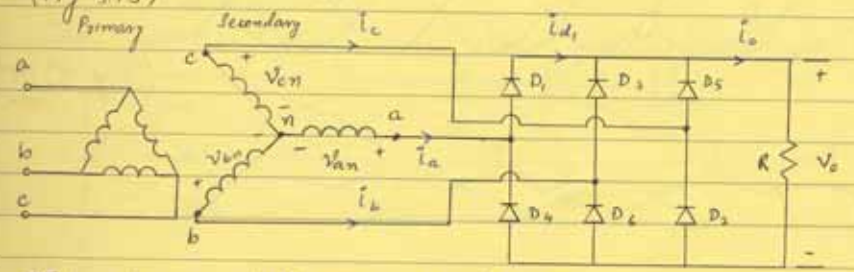

- \* This is a full wave rectifier.
- \* It can be operated with or without a transformer and gives six pulses ripples at output.
- \* Diodes are numbered in order of operational sequence.
- \* Each diode conducts for 120°.
- \* Diodes which are connected into supply lines with highest amplitude of line to line voltage will conduct.
- \* Six ripples per cycle.

\* If  $V_m$  is peak value of phase voltage which is  $V_L/\sqrt{3}$  is given by

$$V_{an} = V_m \sin(\omega t) \quad , \quad V_{bn} = V_m \sin(\omega t - 120^\circ)$$


$$V_{cn} = V_m \sin(\omega t - 240^\circ)$$

\* The line voltages lead the phase voltages by 30° hence expression for line voltages.

$$V_{ab} = \sqrt{3} V_m \sin(\omega t + 30^\circ) \quad , \quad V_{bc} = \sqrt{3} V_m \sin(\omega t - 90^\circ)$$

$$V_{ca} = \sqrt{3} V_m \sin(\omega t - 210^\circ)$$

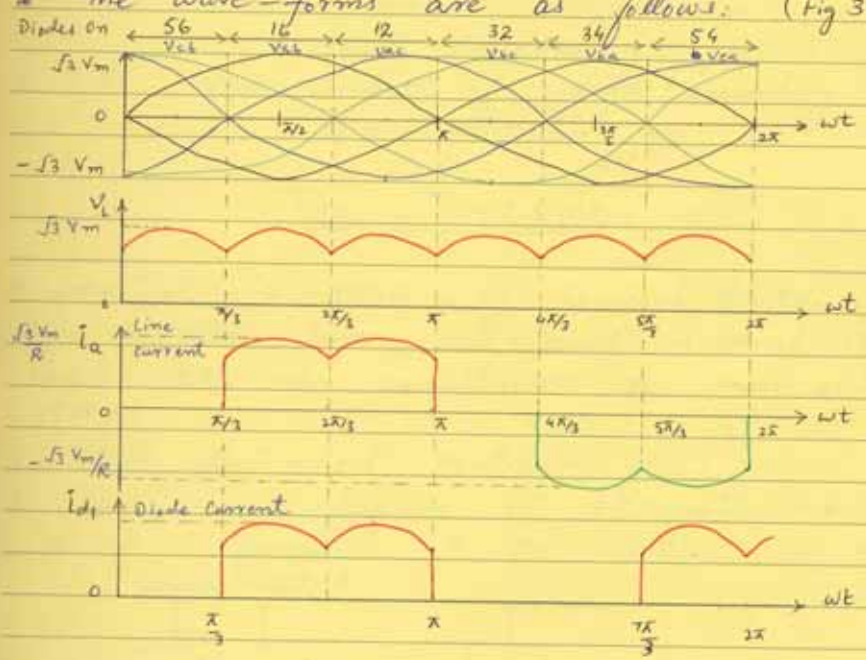\* The wave-forms are as follows: (Fig 3.14)



Conductions  $B \Rightarrow D_3, D_6$  ;  $a \Rightarrow D_1, D_4$

$c \Rightarrow D_5, D_2$

$V_{bc} = D_3, D_6$  ;  $V_{cb} = D_5, D_2$

$V_{ac} = D_1, D_4$  ;  $V_{ca} = D_5, D_2$

$V_{ab} = D_1, D_4$  ;  $V_{ba} = D_3, D_6$

Date 21-02-2008


- \* The average output voltage is  
 $V_{dc} = 1.654 V_m$
- \* The rms o/p voltage is given by:  
 $V_{rms} = 1.6554 V_m$
- \* For a purely resistive load peak diode current is  
 $I_m = \sqrt{3} \frac{V_m}{R}$
- \* The rms diode current is:  
 $I_{rms} = 0.5518 I_m \approx 0.9557 \frac{V_m}{R}$
- \* The rms value of left secondary current is  
 $I_s = 0.7804 I_m$

## THE THYRISTOR

\* Invented in 1957 by General Electric present day thyristor have rating of order of 1500 Amps and 10KV w/c corresponds to power rating of 15MW!

\* Silicon Controlled Rectifier (SCR)

\* Consist of layers of alternate P & N type semi-c forming 3-PN junctions as shown:

 

Date 21-02-2008



- \* When anode is +ve w.r.t cathode, junction A & C are forward biased whereas junction B is reverse biased and hence thy. can't conduct.
- \* Under the anode a forward leakage current is flowing through device.
- \* When anode voltage is further inc'd to a value higher than  $V_{BO}$ , forward leakage current will reach saturation and reverse biased junction will breakdown.
- \* Forward leakage current: Device is off
- \* Avalanche phenomena i.e. reversible in nature.
- \* This is called Avalanche Breakdown.
- \* After breakdown a high fwd current flows thru device w/c can only be limited by external load.
- \* Under this condition voltage drop across device is 1 to 2V.
- \* Thy. shall behave as a conducting diode.
- \* If anode voltage is now dec'd it shall have ~~not~~ no effect on this flowing current as long as it remain higher than latching current ( $I_L$ ).
- \* If now fwd current becomes  $<$  holding current ( $I_H$ ), the depletion layer would again start appearing around junction 'B' & thy. will enter fwd block state.
- \* If rated current is 40A, holding current is about 10mA.

- \* When anode is +ve w.r.t cathode, a small gate voltage can also turn ON thyr as a small gate current starts to flow through layers P<sub>1</sub> and P<sub>2</sub>.
- \* There is no way to stop thyr if it is turned on by gate, it remains on until gate volt is zero, it has no effect on it.
- \* This method of switching is called gate control and perhaps most important method w.r.t thyr operation.
- \* If cathode is made +ve w.r.t anode, junction A and C shall be reversed biased and junction B forward biased. A small leakage current flow thru device & device is called the Reverse (break) Blocking state.

### THE VI Characteristics

(Transfer characteristics)

(Fig 2.2)

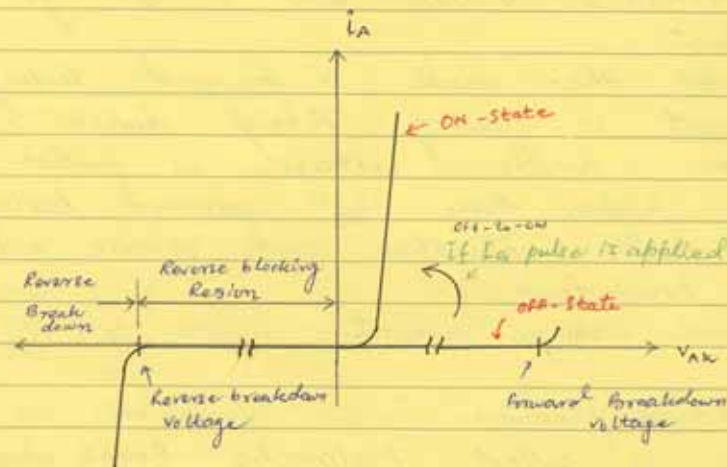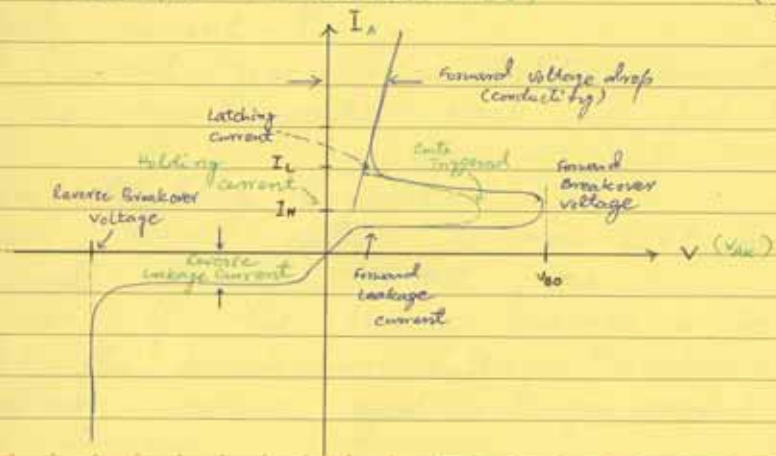


- \*  $I_H$  = holding current to make device ready means device is still conducting.
- \*  $I_L$  = The limit of current where SCR can drive load.

### Regions of Operation

- Forward Blocking ◦ Forward Conducting
- Reverse Blocking.
- Forward Blocking Region:
  - \* The anode is +ve but anode voltage is less than the breakover voltage. A small forward leakage current flows but overall thyrs remain turn-off.
- Forward Conducting Region:
  - \* Anode voltage is greater than breakover voltage
  - \* Thyrs conducts & a large forward current flows.
  - \* The conduction can be achieved much prior to breakdown (over) voltage if the small gate current  $I_g$  is supplied. This would be called "Gate Controlled Turn ON" of the device.
  - \* The forward current must be more than latching current  $I_L$ .
  - \* If current goes below holding current value  $I_h$ . The thyrs switches back to fwd blocking state.
- Reverse Blocking Region:
  - \* Under this cathode is +ve w.r.t anode.
  - \* A small reverse current flows.
  - \* However if this reverse voltage is inc↑ beyond the breakdown voltage (avalanche) breakdown occurs and a large current flows thru device.

### THE TWO TRANSISTOR MODEL OF SCR

\* If we split middle two layers into two separate parts each, as shown below we obtain two transistor model of a SCR.

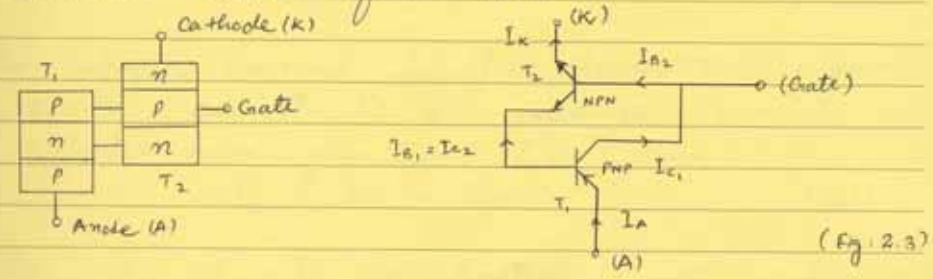

(Fig. 2.3)

- \* One transistor here is npn other is pnp trans.
- \* With no gate signal npn transistor would remain cut-off with almost zero collector current.
- \*  $I_c$  of npn trans. is actually base current for pnp trans. hence under no gate signal thyrs is in forward block mode.
- \* A +ve bias at gate would turn npn trans. ON.
- \* This in turn would establish  $I_c$  of npn trans w/c is  $I_b$  for pnp transistor.
- \* Hence pnp trans. would also turn ON. Now the  $I_c$  of Pnp trans. is actually  $I_b$  for npn.
- \* Thus an inc↑ of current in one trans. causes inc↑ of current in other and this cumulative action turns ON thyristor.
- \* Since  $I_c$  of pnp trans (w/c is also base current of npn) is much larger than gate

Date 21-02-2008.

current, hence once turned on, gate loses control at device and thyr remains conducting even if gate bias is removed!

\* Hence gate bias can only turn ON SCR but it can't turn it off.

\* The collector current  $I_c$  of a transistor is sum of emitter current  $I_E$  & leakage current of collector-base junction  $I_{CBO}$ . Thus

$$I_c = I_E + I_{CBO} \quad (2.1)$$

\* The ratio of  $\frac{I_c}{I_E}$  is denoted by  $\alpha$  is known as "Current gain".

\* For trans.  $T_1$  emitter current is anode current  $I_A$ . Therefore,  $I_{c1}$  of  $T_1$  is

$$I_{c1} = \alpha_1 I_A + I_{CBO1} \quad (2.2)$$

\* where  $\alpha_1$  is current gain of  $T_1$  and  $I_{CBO1}$  is leakage current of collector-base junction of  $T_1$ . Similarly the collector current  $I_{c2}$  of  $T_2$  is

$$I_{c2} = \alpha_2 I_k + I_{CBO2} \quad (2.3)$$

\* where  $\alpha_2$  is current gain,  $I_k$  is emitter current &  $I_{CBO2}$  is leakage current of c-b junction of  $T_2$ . The emitter current of  $T_2$  is  $I_k$ .

From Eq (2.2) & (2.3)

$$I_A = I_{c1} + I_{c2} = \alpha_1 I_A + I_{CBO1} + \alpha_2 I_k + I_{CBO2} \quad (2.4)$$


Moreover

$$I_A + I_G = I_k \quad (2.5)$$

Date 21-02-08

Combining Eq (2.4) & (2.5)

$$I_A = \frac{I_{CBO1} + I_{CBO2} + \alpha_2 I_k}{1 - (\alpha_1 + \alpha_2)} \quad (2.6)$$

 

(Fig 2.4)

(Variation of  $\alpha$  with  $I_E$ )

\* Regenerative or +ve feedback.

\* The junction capacitance affect thy characteristics under transient conditions. Let thy be in fwd blocking state. Fig 2.5 shows junction capacitance. The current  $i_B$  is


$$i_B = \frac{d}{dt} (q_B) = \frac{d}{dt} (C_B V_B)$$

$$i_B = V_B \frac{dC_B}{dt} + C_B \frac{dV_B}{dt} \quad (2.7)$$


(Fig 2.5)

\* Transient Analysis

\* Steady State analysis

 

$$t_p = \frac{t_{on} + t_{off}}{2}$$

 

\* Stray capacitance effects on transient time or have a major role, will be dominant in transient time.

\*  $C_B$  is more > than  $C_A$  &  $C_C$

\* Say  $I_B$  is leakage current of  $j\alpha B$

Stray capacitance depends on several parameters like Anode voltage, cathode voltage ambient temperature.

$$I_B = V_B \frac{dQ_B}{dt} + C_B \frac{dV_B}{dt}$$

\* where  $Q_B$  is charge in junction B and  $C_B$ ,  $V_B$  are junction capacitance & voltage as shown in Fig 2.5. If  $\frac{dV}{dt}$  is high, current  $I_B$  would be high. This would result in an inc<sup>n</sup> in leakage current  $I_{CB01}$  and  $I_{CB02}$  and cause thyrs to turn ON. Moreover, high value of  $I_B$  may even damage the thyrs.

### THYRISTOR TURN ON METHODS


\* Also called "Triggering"

\* Methods are:

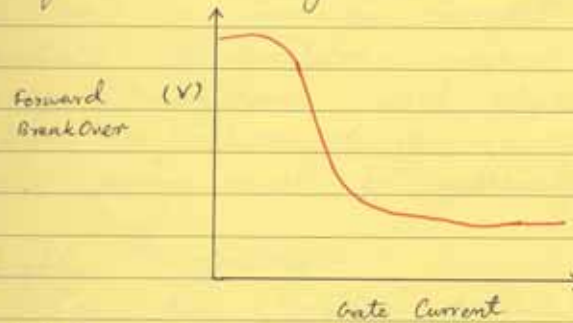- (1) Voltage Triggering
- (2)  $\frac{dV}{dt}$
- (3) Gate
- (4) High Temperature
- (5) Light

\* Voltage Triggering is seldom used as high voltage may destroy Thyrs.

\* In gate + forward breakover voltage shifts with gate current as shown:



\*  $\frac{dV}{dt}$  Triggering:

\* The reverse biased  $j\alpha B$  behaves as a capacitor under forward blocking mode.

\* If a rapidly changing voltage is applied across Anode and Cathode of thyrs, a charging current  $I_B$  flows thru device from A to K. This charging  $I$  directly depends upon rate of change of voltage or Transient voltage as shown by following equation.

$$I_B = C_B \frac{dV}{dt}$$

Date 27-02-2008

- \* Greater voltage transient, greater current  $I_a$  greater forward current. This higher forward current may cause turning on of thyr.
- \* This method is not suitable for SCR triggering either as high  $I_a$  would result in high fwd current that may damage SCR.
- o High Temperature triggering:
  - \* As temperature of a p-n junction inc  $\uparrow$  width of depletion layer sect. This is due to reason that number of electron hole pairs is inc  $\uparrow$  & leakage current inc  $\uparrow$ . At a certain temperature reverse biased junction may breakdown and thyr starts conducting. High temperature triggering may cause thermal run away and is generally avoided.
- o Light Triggering:
  - \* In this method particles (neutrons or photons) are made to strike reverse biased junction. This cause an inc  $\uparrow$  in number of electron-hole pairs and triggering of thyr. This method of triggering is used in light activated silicon controlled rectifier (LASCR) and high light activated silicon switch (LASCS).

Date 22-02-2008

## Gate Control

An easy method to switch ON SCR into conduction state is to apply proper +ve signal to gate. This signal should be applied when thyristor is forward biased and should be removed after device has been switched ON. The turn on time is about 1-4  $\mu$ sec. This gate signal can be dc, ac and pulse.

(28-11-2008)

Gate signal can be: ac signal, pulse, DC voltage

(a) DC Gate Signal: The application of a dc gate signal causes flow of gate current etc triggers SCR. The disadvantage of this method is that signal has to be continuously applied resulting in power loss. Moreover, gate control ckt is not isolated from the main power circuit.

(b) AC Gate Signal: In this method a phase-shifted ac voltage derived from main supplies the gate signal. The instant of firing can be controlled by phase angle control of gate signal.

Natural deactivation of gate

(c) Pulse: In this method SCR is triggered by application +ve pulse of correct magnitude. A power electronics circuit has a number of thyrs connected in series & ||.


= A pulse has a regulated waveform of a fixed duration. It can be +ve or -ve. They have to be switched on at proper

Date 28-02-2008

instants in a certain sequence. This can be done by a train of high frequency pulses applied to proper instant through a logic circuit. A pulse transformer is used for isolation. In this method gate losses are very low b/c drive is discontinuous.
 
### Trigger Current and Trigger Voltage

The actual source voltage needed for triggering depends on gate circuit. In fig 18 gate circuit current  $I_a$  flows through a resistance  $R_g$ . It is seen that



$$V_s = V_g + I_a R_g \quad \dots (29)$$

### Thyristor Specification and Ratings

#### VOLTAGE RATINGS

(a) Peak working off state fwd voltage ( $V_{VDM}$ ): Known as peak working fwd blocking volt, this is ~~min~~ max<sup>t</sup> value of (fwd) volt w/c thy<sub>r</sub> can withstand when it is in off state. All repetitive and non-repetitive transient voltage are ~~exactly~~ excluded from this definition.

(b) Peak repetitive off-state fwd volt ( $V_{ORM}$ ): It is max value of fwd voltage w/c thy<sub>r</sub> can withstand when it is off-state & volt

Date 28-02-2008

is applied repeatedly. This voltage is specified at a max<sup>t</sup> allowable jns temperature. A thy<sub>r</sub> has to withstand such a voltage when it is turned off.

(c) Peak impulse fwd blocking voltage ( $V_{DSM}$ ): It is max value of any non-repetitive surge<sup>t</sup> voltage w/c thy<sub>r</sub> can withstand when is turn-off state.

(d) Peak working reverse voltage ( $V_{RWM}$ ): It is max value of rev. volt w/c thy<sub>r</sub> can withstand. (repetitive and non-rp transient volt. are excluded from this definition.

(e) It is max value of reverse volt. w/c may be applied repeatedly to thy<sub>r</sub>.

(f) It is max. transient rev volt w/c thy<sub>r</sub> can withstand. If a diode having same rating as thy<sub>r</sub> is connected in series with it, the peak voltage across thy<sub>r</sub> is reduced.

(g) On state voltage ( $V_T$ ): It is  $V_{drop}$  across thy<sub>r</sub> (ie  $V_{A-K}$ ) at specified value of fwd current & jns temperature. It is about 1-1.5V.

(h) It is max<sup>t</sup> gate voltage required to cause gate triggering current.

(i) It is max<sup>t</sup> rate of rise of a A. voltage w/c will not trigger thy<sub>r</sub>, if gate smd is



applied. It is evident that  $\frac{di}{dt}$  is more than rated value, thyr may be turned ON. As discussed previously a high  $\frac{di}{dt}$  can turn ON a thyr. even if absence of gate-signal, due to flow of charging current.

(j) Voltage safety factor:

The actual rev. volt across thyr should be less than  $V_{RSM}$  under all conditions of operation. To ensure the device doesn't get damaged, a safety factor of about 2 is used. This safety factor is defined as

$$\text{Voltage safety factor} = \frac{V_{RSM}}{\sqrt{2} \text{ (RMS VP voltage)}}$$

(eg. Jockey potory: medium size) (max-size, 10k-15k) - (2.10)

Tolerances: in long-term or Short-term.

CURRENT RATING

(a) Average on state (fwd) Current ( $I_{TAV}$ ):

Since vdrop across a conducting thyr is low, current  $I_{TAV}$  determines power loss in thyr. For same average current but different conducting periods, peak I and therefore, the jns temperature are different. Therefore, permissible voltage average current should be dec't with inc't in period of conduction. The current  $I_{TAV}$  depends on temperature of case & data sheets of manufactures

indicated this fact.

(b) RMS ON state current ( $I_{RMS}$ ):

Even if actual average value of fwd I is less than specified value, the heating may be excessive. This is bc of reason that heating depends on effective (RMS) current and not average I. Therefore, an rms value of fwd current is also specified for max jns temperature.

(c) Impulse (surge) current rating ( $I_{TSM}$ ):

In addition to rated steady state current a thyr is also subjected to Surge I under abnormal conditions. This current is max. surge I (non-repetitive) w/c thy can withstand.

- + Maximum AC handling capability ( $I_{TSM}$ )
- + " DC " capability ( $I_{TSMDC}$ )

(d)  $I^2t$  Rating:

It is max. non-repetitive value of square of instantaneous current integrated over time. Thus it indicates energy that device can absorb without getting damaged. It is usually specified for overloads lasting less than one half cycle. This rating is necessary co-ordinate working of thyr with operation of a fast acting fuse used to protect thyr against overloads.

Response time -  $I^2t$   
(Fuse rating)

Date 28-02-2008

(e)  $\frac{dv}{dt}$  rating:

This rating indicates maximum allowable rate of inc<sup>t</sup> of anode 'I'. When thyr is triggered, conduction initially starts near cathode and then spreads to whole jct. If  $\frac{dv}{dt}$  is very high, conductivity may not be able to spread as fast and local hot spots may occur. This may raise temperature beyond permissible limit. The safe value of  $\frac{dv}{dt}$  lies in range of 50 to 800 A/ $\mu$ sec. A special type of thyr known as Amplifying Gate Thyristor can withstand very high  $\frac{dv}{dt}$ . Moreover, a thyr using a hard drive gate  $\frac{dv}{dt}$  circuit can withstand high  $\frac{dv}{dt}$ .

(e) Holding Current ( $I_h$ ):

It is max. 'I' at w/c thyr can continue conducting. If anode become less than  $I_h$ , thyr is turned off. This current is in mA range.

(f) Latching Current ( $I_L$ ):

When gate current is applied to a thyr (in fwd blocking mode), 'A' current starts inc<sup>t</sup>. Latching current is min<sup>d</sup> anode 'I' to keep thyr in conducting state after gate pulse is removed. This 'I' is about two to 3 times holding current.

(g) Max &amp; Min Gate current:

The minimum gate current indicates that value of gate current w/c is sufficient to turn ON thyr. The min<sup>d</sup> gate current depends on

Date 28-02-08

rate of rise of 'A' current. The max gate 'I' indicates safe value of gate current. Gate 'I' should not exceed the max value.

## POWER RATINGS

(a) Forward Conduction loss:

The average fwd conduction loss equals product of average 'A' current and  $V_{drop}$  across thyr. For same value of average 'A' current, this loss inc<sup>t</sup> with  $\downarrow$ dec in period of conduction. This loss is a major portion of losses in a thyr.

(b) Turn ON loss:

During turn ON process,  $V_{drop}$  across a thyr is pretty high<sup>is high</sup>. Therefore appreciable power loss occurs during turn ON period.

(c) Turn OFF loss:

During rapid off, reverse current may be as high as fwd conduction 'I'. To limit this loss an extra inductance is added in circuit. However, this inductance may cause high rev. volt transient. In high frequency dets thyr are turned ON and OFF many times in each cycle of mains frequency. In such cases turn ON & OFF losses may be appreciable.

(d) Forward blocking (leakage) loss:

This loss occurs when a fwd volt is applied but thyr is not conducting. A fwd

leakage current flows during this period. It is product of fwd blocking volt & fwd leakage current. This loss is small.

(e) Reverse blocking (leakage) loss:

This loss occurs when rev voltage is applied. It is equal to product of rev. voltage and rev leakage current. This loss is also small.

(f) Gate Power loss: This loss equals product of gate voltage &  $I_g$ . Most thyr. dets use pulse signals for triggering. For such system gate power loss is negligible.

TEMPERATURE Ratings

(a) Junction temperature ( $T_j$ ): The jns temperature determines ability of thyr to operate successfully. If jns temperature goes beyond specified value, thyr may start conducting even if gate signal is not applied. The fwd breakover volt turn off time and thermal stability depends on jns temperature.

(b) Thermal resistance: The heat dissipation from cooling <sup>surface</sup> depends on the thermal resistance it is expressed in unit of temperature difference ( $^{\circ}C$ ) per watt of power dissipated.


Selection of Parameters of Triggering Circuit

Gate characteristics

- \* It is a graph b/w gate voltage ( $V_g$ ) and gate current ( $I_g$ )
- \* Two curves for two extreme conditions are shown below.

\*  $P_g = V_g I_g$

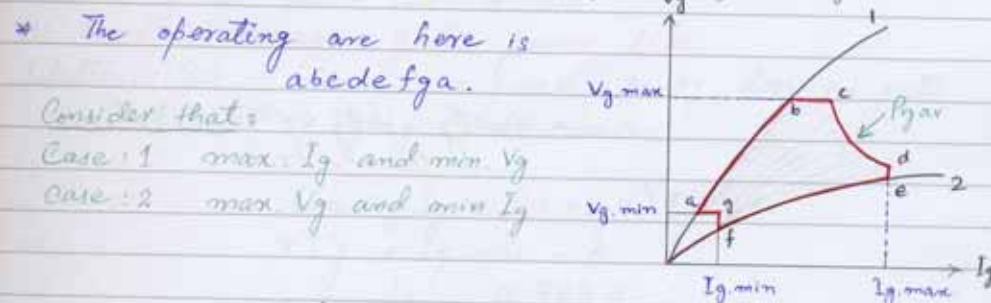\* It is also shown in following diagram:




Consider that:

Case: 1 max.  $I_g$  and min.  $V_g$

Case: 2 max.  $V_g$  and min.  $I_g$

Triggering Circuits

 

\* Fig 2.20(a) show the simplest triggering circuit  $V_s = V_g + I_g R_s$ .

\* Fig 2.20(b) shows triggering circuit after resistance 'R' has been added b/w gate & cathode. This resistance is connected to provide a path for leakage current. Taking min value of  $V_g$  &  $I_g$  as  $V_{g,min}$  &  $I_{g,min}$

Date 05-03-2008

We get

$$V_s = \left( \frac{V_{g, \min}}{R} + I_{g, \min} \right) R_s + V_{g, \min}$$

Example 2.14: The  $V_g - I_g$  characteristics of an SCR is given by  $V_g = 1 + 9 I_g$ . The gate pulses are rectangular with voltage amplitude of 12V and duration 60  $\mu$ sec. The duty cycle is 0.3

(a) Find series resistance  $R_g$  in gate ckt to limit peak power loss to 6W.

(b) Find average gate power loss.

Solutions (a) Since a peak power loss in gate circuit is  $V_g I_g$ , we have

$$6 = V_g I_g = (1 + 9 I_g) I_g$$

$$9 I_g^2 + I_g - 6 = 0$$

$$I_g = 0.763 \text{ A}$$

KVL equation of gate circuit is

$$12 = V_g + R_g I_g = 1 + 9 I_g + R_g I_g = 1 + (9 + R_g) I_g$$

$$11 = (9 + R_g)(0.763)$$

$$R_g = 5.417 \Omega$$


(b) Average power loss =  $6 \times 0.3 \Rightarrow 1.8 \text{ watt}$

Date 06-03-08
 
## Methods of to improve $di/dt$ and $dv/dt$ Ratings of Thyristor

\* Base of construction of SCR is sharing of it

Auxiliary Thyristor to improve the  $di/dt$  Rating:



\* The higher gate current greater current handling capability

\* As resistance of SCR is inversely proportional to Anode to Cathode current.

## Intermixing of Gate & Cathode regions

\* As size of cathode region is large, larger the current capability


\* So gate region is developed within the cathode region

\* So instead of making single gate

in cathode many distributed gates

are added in cathode so di

increase can be handled well

 


Distributed gate config.

## Gate Assisted Turn-off Thyristor

Turn off time: 10  $\mu$ s,  $V_{BO} = 2000 \text{ V}$


On state Current = around 1500 A

 




\* Increase in voltage (A-K) causes leakage current from (G) and no path to flow (dissipate) the leakage current.
 
### Cathode Shorts to increase $dv/dt$ Rating

- \* It is the current that is formed due high voltages at A-K damages the rest not the high voltages
- \* By this technique current have several different ways (external paths) to flow heavily.




### DIODE FOR AC (DIAC)

   

- \*  $V_{BO}$  for common Diac is about 30V.
- \* It only conducts when only  $V_{BO}$  is reached.
- \* Typical application is for triggering Triacs. A triac requires a +ve or -ve pulse to trigger it ON, the diac provides same.
- \* Matched Diac/Triac combinations are manufactured by a number of manufacturers

 Diac: A two terminal, three layer bidirectional device which can be switched from its OFF state to ON for either polarity of applied voltage.





- Operations:
- o when a +ve or -ve voltage is applied across diac, only a small leakage current ( $I_a$ ) will flow through device.
  - o As applied voltage is inc + leakage current will continue to flow until voltage reaches breakover ( $V_{BO}$ ).
  - o At this point avalanche breakdown of reverse-biased jns occurs and device exhibits -ve resistance i.e current through device inc + with dec + values of applied voltage. The voltage across device then drops to break back ( $V_w$ ) voltage.
  - o Note: The breakover voltage and holding current values are identical for forward and reverse regions of operation.



TRIAC (TRIODE FOR AC)

THE Bi-Directional SCR

  

(a)


(b)

- \* It conduct in both direction.  $T_1 \rightarrow T_2$  /  $T_2 \rightarrow T_1$
- \* There is overlapping of Terminals.

First Quadrant Operations:


MODE-1

 - \*  $P_1-n_1$  and  $P_2-n_2$  Forward biased
- \*  $n_1-p_1$  breaks down, normal current starts to flow.
- \* Gate is not biased slightly less than  $T_2$ .



MODE-2


 
- \* Initially:  $P_1-n_1, P_2-n_2$
- \* After current flow  $P_1-n_1, P_2-n_2$



Third Quadrant Operations:

MODE-3

  - \*  $P_2-n_1, P_1-n_2, n_1-p_1$  breaks down current starts to flow thru above path.
- \* Third quadrant operation high gate




\* The supply voltage at w/o triac is turned ON depend upon gate current  $I_g$ . The greater gate current in smaller supply voltage at w/o triac is turned ON.

\* Advantages: The feature of reason to use this is that by adjusting gate current to a proper value any portion of +ve and -ve half cycle of ac supply can be made to flow through load. This permits to adjust transfer of a.c. power from source to load.


Date 06-03-2008

MODE - 4

 
- \* P<sub>2</sub>-n<sub>1</sub>-P<sub>1</sub>-n<sub>4</sub>, n<sub>1</sub>-P<sub>1</sub> breaks down current starts to flow thru above path.
- \* 3<sup>rd</sup> quadrant operation lesser gate current is required to turn-ON triac. Its more sensitive in this mode.



V-I characteristics

 

SCR MOUNTINGS

 

Date 06-03-2008

Thermal Ohm's Law

The heat dissipation is governed by thermal ohm's law. As per analogy with electric circuit theory, temperature difference is analogue to voltage difference, heat is analogue to charge and thermal resistance is analogue to electrical resistance.

As per thermal ohm's law, heat dissipation is given by

$$\theta_{21} = \frac{T_2 - T_1}{P_{21}}$$

- where  $\theta_{21}$  = Thermal resistance b/w point 2 & 1.
- $P_{21}$  = Power loss to be dissipated from ".
- $T_2$  = Temperature of point 2, °C.
- $T_1$  = " " " " 1, °C.

Calculation of Thermal Resistance:

\* The thermal resistance of material is given by

$$\theta = \frac{l}{\lambda A}$$

- where  $\theta$  = thermal resistance  $\theta$  °C/W
- $A$  = Cross-sectional area, m<sup>2</sup>
- $l$  = length, m
- $\lambda$  = Thermal conductivity, W/m°C.

\* A material used commonly for heat sinks is 90% aluminium having conductivity of 220 W/m°C.

HEAT SINKS

- \* Greater no. of fins, greater the volume, greater heat dissipation.
- \* Today Aluminium alloys are formed.
- \* Heat sink should be light in weight.
- \* Should not melt with high temperature increase.

Example 2.17: Find thermal resistance of square cross section aluminium rod having length 0.2m width 0.01m and depth 0.01m. Thermal conductivity is 220 W/m°C. If temperature at far end is 30°C find temperature of surface where heat is injected and cube has power dissipation of 3 watt?

Solution: Thermal resistance

$$\theta = \frac{0.2}{220 \times 0.01 \times 0.01}$$

$$\theta = 9.091 \text{ } ^\circ\text{C/W}$$

$$T_2 = (P)\theta + T_1$$

$$= (3)(9.091) + 30^\circ$$

$$T_2 = 57.27^\circ\text{C}$$

Example 2.18: An electronic device is mounted on an aluminium plate having length 2mm and area of cross section 120 cm<sup>2</sup> it is desired that temperature drop along 2mm length should be 4°C. Take thermal conductivity of Al as 220 W/m°C. Find max losses w/c can be handled by module.

Practice Assignment:

- Q/ Assume that for same heat sink module:
- (A) The volume inc<sup>r</sup> 3 times.
  - (B) " " dec<sup>t</sup> 3 times.

\* Evaluate (comment) on the changes in electrical loss (P) and thermal resist.  $\theta$  for the two cases. \* \* \*

Q Example 2.19: A thyr has a power dissipation of 30W. Assume max junction temperature 125°C and max ambient temperature of 50°C. The thermal resistance of thyr is 1°C/W. The device uses a 65 μm thick mica insulator having thermal R of 0.3°C/W. Find thermal resistance of heat sink and select a proper heat sink.

Solution:

$$\text{Total thermal } R = \frac{\text{Temperature diff}}{\text{Power dissipated}} = \frac{125-50}{30}$$

$$= 2.5 \text{ } ^\circ\text{C/W}$$

$$\text{Thermal resistance of heat sink} = 2.5 - 1 - 0.3$$


$$= 1.2 \text{ } ^\circ\text{C/W}$$

Heat sink no. 10 in fig. 32 has a thermal resistance of 1.2°C/W and is suitable for this purpose.



### Triggering Circuits


#### Resistance Triggering Circuit

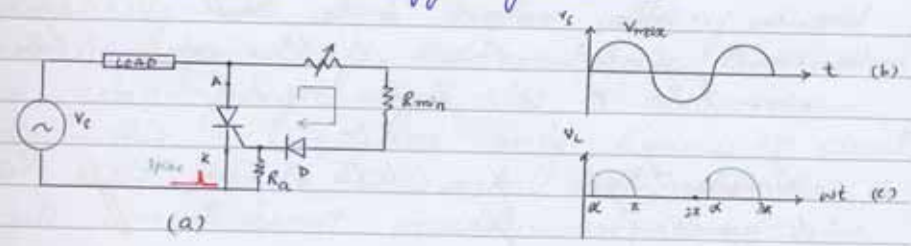

1. When voltage  $V_s$  starts its +ve half cycle, thyristor become fwd biased. However it start conducting only when its gate current  $I_g$  min exceed. During this +ve h.cycle Diode G-k jct of SCR also become fwd biased.
2. As  $V_s$  inc $\uparrow$ ,  $I_g$  current inc $\uparrow$ ,  $I_g$  becomes more than  $I_{g(min)}$  SCR start conducting. when SCR conducts, v.drop across it is very small. Therefore almost total voltage  $V_s$  appears across load.
3. SCR continues to conduct till current thru it is more than holding current. Since holding current is very small (a few mA only). SCR conducts almost ( $\omega t = \pi$ ).
4. At  $\omega t = \pi$ , a reverse voltage appears SCR and it turns OFF.
5. The diode in G-ckt does not allow G-k reverse bias To exceed peak rev. voltage during -ve h.cycle. PIV rating of diode should

become more than  $V_{max}$ . (At least twice).  
 \* The firing angle  $\alpha$  can be controlled by varying  $R$ . If  $R$  is more,  $I_g$  will attain value  $I_{g(max)}$  at a higher value of  $\alpha$  and conduction period of SCR would be lower, when  $R$  is zero, firing angle  $\alpha$  is also min. Under this condition only  $R_{min}$  is in circuit. The  $R_{min}$  should be such that, when  $R=0$ , the gate current doesnot exceed max allowed value.

#### RC Triggering Circuit 'Half Wave'

 

- \* Variable  $R$  &  $C$  adjust time constant or Turn On Time of SCR!
- \* During -ve h.cycle of  $V_s$ , Cap charges to  $V_{max}$  with lower plate +ve through diode  $D_2$ . The volt across  $C_{cap}$  is equal to  $V_{max}$  at  $\omega t = 90^\circ$ . The cap voltage remains at this value (or may dec $\downarrow$  slightly) as source voltage changes from  $V_{max}$  at  $\omega t = -90^\circ$  to zero at  $\omega t = 0$ .  $V_s$  starts its +ve h.cycle, cap starts charging rev direction

Date 12-03-2008.

through resistance  $R$ . The rate of charging of cap in +ve h.c. is controlled by  $R$ . when volt across cap has become +ve and equal to  $V_{g(min)} + V_{D1}$  (where  $V_{D1}$  is v. drop across  $D_1$ ). SCR is triggered, after caps voltage remain at this same value during remaining +ve h. cycle. In next cycle process is repeated.  $D_1$  prevents rev breakdown of gate.

An empirical relation for product  $RC$  is  $RC \geq 0.65 T$

where  $T = \frac{1}{f}$  time period of supply voltage.

Since  $T = \frac{2\pi}{\omega}$ , we get

$$RC \geq 0.65 T = \frac{0.65(2\pi)}{\omega} = \frac{4}{\omega} \quad (2.18)$$

SCR will trigger when cap voltage  $V_c$  is  $V_c = V_{g(min)} + V_{D1}$ . The instantaneous value of  $V_s$  at instant of triggering is


$$V_s \geq (I_{g(min)} \times R) + V_{g(min)} + V_{D1}$$

$$R \leq \frac{V_s - V_{g(min)} - V_{D1}}{I_{g(min)}} \quad (2.19)$$

The values of  $R$  &  $C$  can be found from eq 2.18 and 2.19.

Date 12.03.08

### RC Turn ON 'Full wave Type'

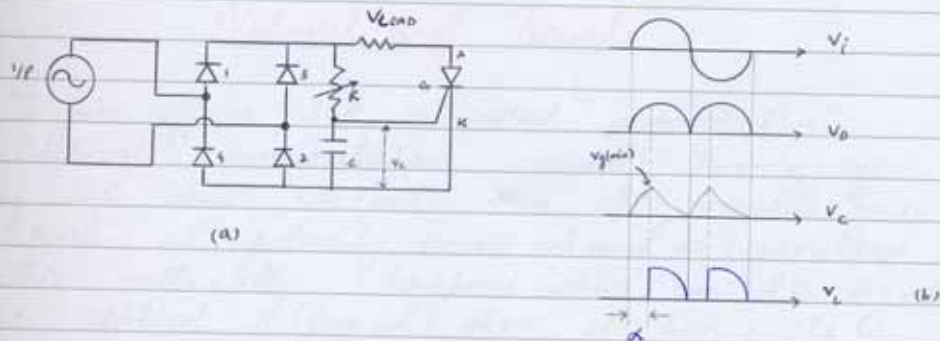

During +ve h.c diode 1 and 2 conducts. During -ve h.c diode 3 and 4 conducts. Thus we get bridge o/p  $V_s$  as shown in fig 2.39 (b). This voltage charges cap 'C' through variable  $R$ . The voltage across cap  $V_c$  as in figure. when value of  $V_c$  reaches a value equal to min gate trig voltage, there is trig in each half cy. The firing angle  $\alpha$  can be controlled by varying ' $R$ '. The load voltage  $V_L$  is also shown. Since there is no diode across resistance in this case eq (2.19) calculating value of  $R$  changes to.


$$R \leq \frac{V_s - V_{g(min)}}{I_{g(min)}} \quad (2.19)$$

### Commutation of SCR's

#### "Natural and Forced"

- \* To turn off a SCR is called "commutation"
- \* Natural commutation means turning off of SCR when current thru it reaches zero level or polarity across B and K reverses. This naturally happens when an AC signal is applied (passed) thru it hence its called natural commutation.
- \* Forced commutation means turning off SCR thru external circuitry.
- \* Components inductances & capacitances are used to attain forced commutation and hence are called "commutating components"
- \* Forced comm. can be classified into class A, B, C, D and E depending upon arrangement of commutating elements used to achieve comm. and method of to achieve zero current and reverse voltage across SCR to turn it off.
- \* Classification is based on config of components and circuit or config of 'C' and 'L' in circuit defines class of circuit.
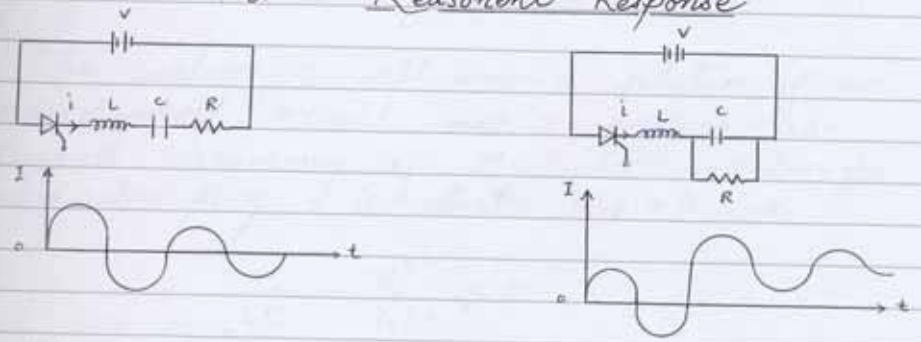
### Commutation of SCR's 'Class - A' or Resonant Response



- \* Identification of class A is that max load current flows thru comm. components as series circuit of comm. components is made.
- \* Oscillator is found to cross zero.

Case 1: when load is in series with L & C.

$$i = \frac{V - V_0}{\omega_d L} e^{-\zeta \omega_d t} \sin(\omega_d t) \quad (2.25)$$

The current reaches zero at

$$\omega_d t_0 = \pi \text{ or } t_0 = \frac{\pi}{\omega_d} = \frac{\pi}{\omega \sqrt{\left(\frac{1}{LC} - \frac{R^2}{4L^2}\right)^{0.5}}} \quad (2.26)$$

where

$$\omega_n = \frac{1}{\sqrt{LC}} \text{ := natural frequency.}$$

and

$$\zeta = \frac{R}{2\sqrt{LC}} \text{ := damping ratio}$$

and

$$\omega_d = \omega_n \sqrt{1 - \zeta^2}$$

\* When current is zero at time  $t_0$ , com. of thyr can take place.

The analysis is well known solution of an underdamped circuit.  $\omega_d$  is known as damped frequency of osc. The condition for underdamping is that  $\omega_d > 0$  or

$$\frac{1}{LC} - \frac{R^2}{4L^2} > 0$$

or

$$R < \sqrt{\frac{4L}{C}} \quad (2.27)$$

Case 2: when load is in parallel with C.

$$i = \frac{V}{\omega_d L} e^{-\zeta \omega_n t} \sin(\omega_d t) + \frac{V}{\omega_n R L C} e^{-\zeta \omega_n t} \left[ \frac{-\zeta \omega_n \sin(\omega_d t) - \omega_d \cos(\omega_d t)}{\omega_n^2} \right]$$

where  $(A = \omega_d t)$  (2.29)

where  $\zeta = \frac{1}{2R\sqrt{CL}} = \text{damping ratio}$


$$\omega_n = \frac{1}{\sqrt{LC}}$$

and

$$\omega_d = \omega_n \sqrt{1 - \zeta^2}$$

Fig shows waveform of current. At a certain time current reaches zero value & com. thyr can be done.
 
### Commutation of SCR, 'Class - B' or Self Commutation



\* In this class no max load current flows thru com. components (Diff b/w class A & B)

\* Initially capacitor gets charged to battery 'V' with upper plate +ve. As soon as thyr is turned on, it starts conducting and supplying current to load 'R'. Now cap starts discharging through L and thyr (The path of this I is thru Thyr, L and back to C). After getting completely discharged, it starts getting charged with opposite polarity (i.e lower plate +ve) B/c of this rev volty a -ve current starts flowing. This -ve current opposes load current. At point 'a' in fig (b) load current and -ve com. 'I' are equal and thyr is turned off. Once thyr is turned off cap starts getting charged again (thru L & R) with upper plate +ve, thus SCR remains off for some time, then remains on for some time & this cycle is

Date 13-03-2008

is repeated. The time for On & off on value of  $L$  &  $C$ .

\* It is seen that both class A and B comtn methods are similar to some extent. The main diff is that in class A, comtn elements carry load but in class B this is not so,

$$\bar{i} = \frac{V}{\frac{1}{JLC} L} \sin\left(\frac{1}{JLC}\right)$$

$$i = V \sqrt{\frac{C}{L}} \sin\left(\frac{1}{JLC}\right) \quad (2.32)$$

The peak value of comtn current is

$$I_c(\text{peak}) = V \sqrt{\frac{C}{L}} \quad (2.33)$$

The Cap voltage is


$$V_c = V \left(1 - \cos \frac{1}{JLC}\right) \quad (2.34)$$

\* After a time  $t = t_0 = \pi \sqrt{LC}$  charging current becomes zero and thyr is switched off, the waveforms of  $I$  and  $V_c$  are shown in fig (b).

\* Due to inductive voltage of ckt can be greater the supply voltage that's way  $L$  is added in ckt.

Date 13-03-2008

## Auxiliary Commutation 'Class C'

 

\* Assume cap is initially charged to  $V_c$  with upper plate +ve and lower -ve.

\* MODE 1: When main thyr is trigd,  $I_L$  thru load flows, mean while cap also begins to discharge thru D,  $Th_1$  and  $L$ .

\* At end of this mode Cap is charged to opite polarity. The diode D prevents its discharging in opt. polarity.

\* MODE 2: For turning off main thyr, aux thyr is triggered.

\* This allows opst. charged cap to get discharged thru main thyr  $Th_1$ .

\* While doing so, current flows thru cathode to A of main thyr.

\* This turns off main thyr.

\* As main thyr ceases conduction, rev current also stops and hence aux thyr also stops.

\* At end of this mode Cap is charged in original polarity i.e. upper plate +ve and lower -ve and cycle repeats.

when  $T_{H1}$  is turned ON, oscillatory current thru C, D and L is given by

$$i_c = \sqrt{\frac{C}{L}} \sin t \sqrt{LC} \quad (2.36)$$

$$\text{Peak cap \& amp; current} = \sqrt{\frac{C}{L}}$$


\* This current must be  $<$  max current of  $T_{H1}$ . If this max current is denoted by  $I_{max}$  we have

$$\sqrt{\frac{C}{L}} < I_{max}$$
  
$$L > \frac{V^2 C}{I_{max}^2} \quad (2.37)$$
 
### Complementary Commutation 'Class D'

MODE 1:

Thy<sub>2</sub>  $T_{H1}$  is turned ON by a gate pulse. Load current flows from battery to load 1 thru  $T_{H1}$ . Along with a cap charging current flows from battery thru load 2, cap and thy<sub>2</sub>  $T_{H1}$ . This current charges cap to battery voltage  $V$  with polarity as shown in fig.



MODE 2: A gate pulse is applied to thy<sub>2</sub>  $T_{H1}$  turning it ON. The cap voltage now appears as rev bias across  $T_{H1}$  and a charging current flows from battery thru load 1, cap and load 2. This charging current charges to cap to  $V_s$  with rev voltage (rev polarity)

when thy<sub>2</sub>  $T_{H1}$  is turned ON in next cycle, volt across cap rev biases thy<sub>2</sub>  $T_{H1}$  and turn it off. The action of events is repeated in subsequent cycle.


$$t_{off} = R_1 C \ln 2$$

Precautions:  $V_c$  should be  $\geq V_s$  to turn off  $T_{H1}$ , otherwise no use of this technique
 
### External Pulse Commutation 'Class E'

MODE 1:

Thy<sub>2</sub>  $T_{H1}$  is turned ON. It supplies load from voltage source 'V'.



At the same time  $T_{H2}$  is also turned ON. A current pulse having a peak value  $V_s \sqrt{C/L}$  flows from source  $V_s$  thru  $T_{H2}$  and L and charges cap to  $2V_s$ . The no. of LC sections can also be more than one. If 'n' is no. of LC sections duration

of current pulse will be  $n\pi\omega C$ . when cap is charged, charging current decr to zero and the thyr  $T_{H3}$  is turned off.


MODE 2: Thyr  $T_{H2}$  is trigd. The cap voltage appears (across) as ser bias at  $T_{H1}$  and turns it off. The capacitor discharges thru load.

The above two mode are repd in each cycle.

### Line Commutation 'Class F'
 
#### CAUTION!

The turn off time of thyr must be less than negative half cycle.




## Protection of Thyristors

\* Reasons:

- A SCR has to be protected from:
  - \* Over Current
  - \* " Voltage
  - \* High  $dv/dt$
  - \* "  $di/dt$ .

(a)  $di/dt$  Protection:

Fig 2.51 shows a simple chopper circuit in etc a fixed dc voltage  $V$  is converted into a variable dc voltage by controlling the ON & off periods of thyr. The  $di/dt$  in circuit can be controlled by including an 'L' in ckt. The max  $di/dt$  in circuit is

 

$$\frac{di}{dt} = \frac{V}{L} \quad (2.43)$$

#### Precautions:


In-appropriate value can inc r losses power losses.

(b) Overvoltage Protection:

\* why over voltage occur in circuit?

Causes of Over-voltage:

 - \* Thyr Commutation
- \* Current Chopping
- \* Lightning
- \* Trfr in-rush current



1. Thyristor Commutation:

when a thyr turn off, a reverse current flows to sweep away the stored charge. This reverse current inc to its max value  $\frac{1}{2}$  then decays at a high rate. This high  $\frac{di}{dt}$  induces a high over voltage  $L \frac{di}{dt}$  to circ 'L'. It has been found that this over-v may be much higher than rated value and may damage thyr.

2. Current Chopping:

when a small current is interrupted by a ckt breaker, current may be brought to zero abruptly and ahead of normal current zero. This known as Current Chopping and is often observed when no load current of a trfr is switched off. Current chp often leads to dangerous over voltages.

(Diagram)

3. Lightning:


HVDC systems are fed by high voltage transmission lines. Atmospheric lightning causes high magnitude over-v w/c travel on lines as travelling waves. When these waves reach converter station HVDC system, thyristor in converter station may be subjected to these over-voltages.

4. Transformer in Rush Current:

when a trfr is switched ON initial magnetising current may be higher than steady state value of  $I_{mag}$  current. If a thyr circuit is connected on secondary side of trfr, thyr may be subjected to over-voltage b/c trfr sec. voltage b/c of in-rush magnetising current may be upto about twice rated sec voltage.

(b) Over voltage Protection:

$$i = k V^\alpha \tag{2.44}$$

 


\* Voltage Dependent Resistor



 (c) Snubber Circuit : dv/dt Protection

When circuit of fig 2.52 is switched on at t=0 cap behaves as a short ckt (b/c voltage across cap can't change instantaneously). Moreover, thyr is in fwd blocking state and has therefore a very high resistance. Therefore, only resistances R and RL & L in ckt.



Hence KVL equation is

$$V = (R + R_L)i + L \frac{di}{dt}$$

(Condition: valid for very short time)

The voltage across thyr at u Ri:

i.e  $V = R i$

or

$$\frac{dv}{dt} = R \frac{di}{dt}$$

$$\left(\frac{dv}{dt}\right)_{max} = R \left(\frac{di}{dt}\right)_{max} = \frac{V}{L}$$

or

$$R = \frac{L}{V} \left(\frac{dv}{dt}\right)_{max} \quad \dots (2.50)$$

The ckt consisting of R, RL, L & C is

always designed to be critically damped. For a critically damped ckt parameters are required as:

$$R + R_L = 2 \sqrt{\frac{L}{C}} \quad (2.51)$$

→ The values R & C can be found from Eqns (2.50 and 2.51)

\* Snubber is a form of critically damped system as critically damped system has fastest response.

\* In an AC ckt parameters L and C can be found from eqs (2.50 and 2.51) by substituting Vmax value of voltage in place of V.

A useful formula to find C is

$$C = 10 \frac{V_A}{V_s^2} \left(\frac{60}{f}\right) \quad (2.52)$$

where

VA := Full load rating of ckt

Vs := Applied voltage

f := Frequency (Hz)

\* Resistance of Snubber


$$R = 2 \sqrt{\frac{L}{C}} \quad \dots (2.53)$$

$L =$  Effective inductance

when max value of  $\frac{dv}{dt}$  is specified,  $C$  is given by

$$C = \frac{1}{2L} \left[ \frac{0.564 V_m}{\frac{dv}{dt}} \right] \quad (2.54)$$

(d) Gate Protection :

 

Example 2.26. In an AC ckt using thyx having  $\frac{dv}{dt}$  25 V/ $\mu$ s, source  $L = 0.2$  mH. The rms value of  $V_s = 230$  V. If damping factor is 0.65 find value of  $R$  &  $C$  of snubber circuit.

Sol

$$V_m = 230 \times \sqrt{2} = 325.27 \text{ V}$$

$$L = 0.2 \times 10^{-3} \text{ H}$$

$$\frac{dv}{dt} = 25 \text{ V}/\mu\text{s} = 25 \times 10^6 \text{ V/s}$$

$$\zeta = 0.65$$

using eq (2.54)

$$C = \frac{1}{2 \times 0.2 \times 10^{-3}} \times \left[ \frac{0.564 \times 325.27}{25 \times 10^6} \right] = 184.6 \times 10^{-6} \text{ F}$$

Example 2.27:  $V_s = 300$  V  $R_L = 10 \Omega$ ,  $L = 0$

$$f = 2000 \text{ Hz} \quad \frac{dv}{dt} = 100 \text{ V}/\mu\text{s}$$

$$I = 100 \text{ A} \quad \text{(a) } R = ? , C = ?$$

(b) power loss. (c) power rating of snubber.

Sol

(a) By KVL eq during charging of cap  $C$  (fig 2.5d) is

$$V = (R + R_L)i + \frac{1}{C} \int i dt + V_C(0)$$

As  $V_C(0)$  is zero,

$$\text{So, } i = \frac{V e^{-t/(R+R_L)C}}{R+R_L}$$

The fwd voltage across thyx is

$$V_{Th} = V - R_L i = 300 - \frac{10 V e^{-t/(R+R_L)C}}{R+R_L}$$

At  $t = 0$

$$V_{Th} = V - \frac{R_L V}{R+R_L}$$

At  $t = \tau = (R+R_L)C$

$$V_{Th} = V - \frac{0.369 R_L V}{(R+R_L)}$$

$$\frac{dv}{dt} = \frac{V_{Th}(\tau) - V_{Th}(0)}{\tau} = \frac{0.632 R_L V}{C(R+R_L)^2}$$

$$R = \frac{300}{100} = 3 \Omega$$

$$\frac{dv}{dt} = 100 \times 10^6 = \frac{0.632(10)(300)}{C(3+10)^2}$$

$$C = \frac{0.632(10)(300)}{13^2 \times 100 \times 10^6} = 0.112 \times 10^{-6} \text{ F}$$

(a)  $C = 0.112 \mu\text{F}$

Example 2.30:  $R = 4 \Omega$ ,  $L = 6 \mu\text{H}$ ,  $C = 6 \mu\text{F}$   
 $V = 300\text{V}$  find max permissible values  
of  $\frac{dv}{dt}$  &  $\frac{di}{dt}$ ?

$$\frac{di}{dt}_{\text{max}} = \frac{V}{L} = \frac{300}{6 \times 10^{-6}} = 50 \times 10^6 \text{ A/s}$$

when ckt is switched ON rate of change  
of voltage across cap is

$$\frac{dv_c}{dt} = R \frac{di}{dt} + \frac{I_{sc}}{C}$$

$$I_{sc} = \text{short circuit current} = \frac{300}{4} = 75\text{A}$$

$$\frac{dv_c}{dt} = 4 \times 50 \times 10^6 + \frac{75}{6 \times 10^{-6}}$$

$$\frac{dv_c}{dt} = 212.5 \times 10^6 \text{ V/s}$$


Hence max permissible value of  $\frac{dv}{dt}$   
 $212.5 \times 10^6 \text{ V/sec}$ .

# Thyristors in Series

Methods available:


- \* Simultaneous.
- \* Sequential.
- \* Optical

## Simultaneous Triggering

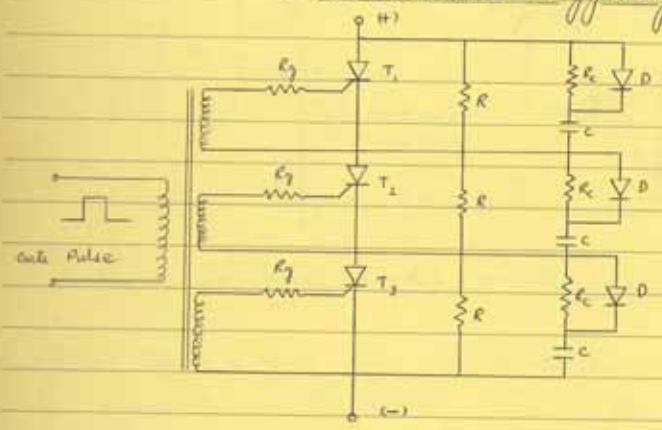

- \* Pulse Transformer: Allows pulse to transform.
  - Core is special
  - Small in size relatively.
- \* A specialized transformer is needed for this method.
- \* Tappings required as no of thyrs are in ckt.

### Sequential Triggering

 

$$0^{PI} C_3 + R_{C3} - R_{g2} - T_2(a-k) - T_3(a-k) - C_3$$

$$0^{PI} C_2 + R_{C2} - R_{g1} - T_1(a-k) - T_2(a-k) - D_2' - C_2$$

\* Above two path of Discharge current  $I_1$  and  $I_2$  causes  $T_2$  and  $T_1$  to trigger.  
 \* In this method Capacitor is most sensitive.

$$C \geq \frac{10}{R_g + \frac{E_{GT(max)}}{I_{GT(max)}}} \mu F \quad (4.10)$$

where,

- $E_{GT(max)} :=$  Max gate trig Voltage
- $I_{GT(max)} :=$  " " " Current
- $R_g :=$  gate-source resistance.


### Optical Triggering

Diagram

\* LASCR. Problem - Electrostatic charge these should be separated electrostatically.

 
### Thyristors in Parallel

\* In case  $T_1$  is off (say) the connection from  $T_2(a)$  to  $T_1(a)$  from Diode (D) insured that  $T_1$  is switched ON.




\* Diode ensures that if  $T_1$  tends to turn off (may be due to its anode current becoming lesser than  $I_H$ ) it will be ON again by  $V_a$  across  $R_2$ .

Date

 

Two problems:

- (1)  $\frac{di}{dt}$
- (2) Load division.

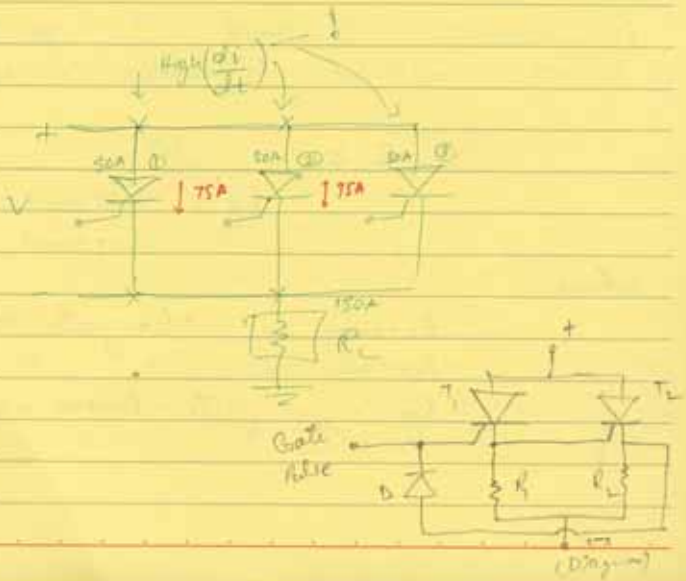

Date 27.03.2008

## AC VOLTAGE CONTROLLERS (Ac Regulators)

- \* O/P voltage < I/P voltage (For this Topic)
- \* It converts an AC voltage in variable AC voltage of same frequency.

\* Applications:

- Industrial heating.
- Illumination level controller. (Dimmer)
- On load txfr tap changing
- Speed control of induction motor.

\* Older alternative methods for AC voltage level control:

- 1x Auto txfr.
- 2x Tap changing txfr.
- 3x Saturable reactance.

\* Advantages of Thyr or triac based AC controllers:

- ↳ High  $\eta$
- ↳ fast Control
- ↳ Compact size.

\* The only dis-advantage however is that they introduce Objectionable harmonics in circuit!

Date 27.03.2008

- \* Classification of AC controllers:
- (1) Single  $\phi$  (Half or Full wave)
  - (2) 3 $\phi$  ( . . . )

\* Single  $\phi$  are actually Unidirectional and full wave are bi-directional.


\* Natural commutation is seen in AC controllers, no need of forced commutation.

\* Types of AC controllers:

- (1) Integral cycle control (ON/OFF)
- (2) Phase control.
 
### Principle of Integral Cycle Control

- \* This method is also called 'ON/OFF control'.
- \* AC supply connected to load for some cycles and it is disconnected from load for another no. of cycles.
- \* On and off times consist of an integral no. of cycles.
- \* Zero crossing Gate turn on is adopted.





(a)

Date 27.03.2008

Let 'ip' voltage be  $V_i = V_m \sin \omega t$

The rms value of off voltage is
  
$$V_L = \left[ \left( \frac{n}{n+m} \right) \frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \omega t d\omega t \right]^{0.5}$$



$$V_L = \frac{V_m}{\sqrt{2}} \left( \frac{n}{n+m} \right)^{0.5}$$

$$V_L = V \sqrt{\alpha}$$



\*  $V_L$  and  $V$  are rms values of off and 'ip' voltages

↳ The ratio  $\left( \frac{n}{n+m} \right)$  is duty cycle 'd'.

- \* It is customary to keep sum  $n+m=100$ .
- \* Method suitable for loads having high mechanical inertia and high thermal constant like industrial heating and speed control of motors.
- \* Period of control is  $(n+m)T$  where  $T$  is time period of AC cycle.
- \* This period should be less than mechanical or thermal time constant.

Example 6.1: An ac voltage regulator uses integral cycle control. The thyrs conduct for 36 cycles and remain off for 64 cycles. The rms value of i/p = 150 V and load resistance is 8 Ω. Find:  
 (a) rms  $V_L$  (b) o/p Power (c) i/p power  
 (d) i/p power factor (e) average and rms value of thyrs current. Neglect losses.

As

$$V_L = \frac{V_m}{\sqrt{2}} \left( \frac{n}{n+m} \right)^{0.5}$$

$$V_L = V_{rms} \left( \frac{n}{n+m} \right)^{0.5}$$

$$= 150 (0.6)$$

$$V_L = 90 \text{ V}$$

(b) Power o/p =  $\frac{(90)^2}{8} = 1012.5 \text{ W}$

(c) neglecting losses o/p power = i/p power = 1012.5 W

(d) RMS Current (load) =  $\frac{90}{8} = 11.25 \text{ A}$

$$VA = 150 \times 11.25$$

$$= 1687.5 \text{ VA}$$

$$\text{Input Pf} = \frac{1012.5}{1687.5} = 0.6 \text{ Lagging}$$

(e) Peak thyrs current =  $\frac{\sqrt{2} \times 150}{8}$   
 $= 26.5165 \text{ A}$

$$\text{Average thyrs current} = \frac{\alpha}{2\pi} \int_0^{\alpha} (26.5165) \sin \omega t d(\omega t)$$


$$= \frac{0.36 \times 26.5165}{\pi}$$

$$= 3.038 \text{ A}$$

$$\text{RMS SCR I} = \frac{26.5165 \sqrt{0.36}}{2}$$

$$= 7.954 \text{ A}$$

### Single $\phi$ Half-wave Ac Controller

 

Date 27.03.2008

Input voltage is  $V_i = V_m \sin \omega t$

The average o/p voltage is given by:

$$V_{av} = \frac{1}{2\pi} \left[ \int_{\alpha}^{2\pi} V_m \sin \omega t \, d(\omega t) \right]$$

or

$$V_{av} = \frac{V_m}{2\pi} (\cos \alpha - 1)$$

The rms value of o/p voltage is

$$V_L = \left[ \frac{1}{2\pi} \int_{\alpha}^{2\pi} V_m^2 \sin^2 \omega t \, d(\omega t) \right]^{0.5}$$

or

$$V_L = \left[ \frac{V_m^2}{4\pi} \int_{\alpha}^{2\pi} \frac{1 - \cos 2\omega t}{2} \, d(\omega t) \right]^{0.5}$$

\*

$$V_L = V_m \left[ \frac{1}{4\pi} \left( 2\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{0.5}$$

Example 6.2: A single  $\phi$  h.w regulator

$V_m = 150V$ ,  $R_L = 8$ ,  $\alpha = 60^\circ$  in each +ve h. cycle. Find (a)  $P_{av}$  (b)  $V_{rms}$  o/p

(c) Power o/p (d) l/p Pf (e)  $I_{av}$  over 1 cycle.

sl

$$V_m = \sqrt{2} \times 150 = 212.1V$$

(a)

$$\begin{aligned} \text{Average o/p voltage} &= \frac{212.1 (\cos 60^\circ - 1)}{2\pi} \\ &= -16.878V \end{aligned}$$

Date

$$\begin{aligned} V_L &= 212.1 \left[ \frac{1}{4\pi} \left( 2\pi - \frac{60^\circ}{180} + \frac{\sin 120^\circ}{2} \right) \right]^{0.5} \\ &= 142.45V \end{aligned}$$

(c) Power o/p =  $\frac{142.45^2}{8} = 2536.50W$


(d) o/p Current = l/p current =  $\frac{142.45}{8} = 17.806A$

$$\begin{aligned} \text{l/p VA} &= 150 \times 17.806 \\ &= 2670.9VA \end{aligned}$$

$$\begin{aligned} \text{l/p Pf} &= \frac{2536.50}{2670.9} = 0.949 \\ &\approx 0.95 \text{ Lagging} \end{aligned}$$

(e) Average l/p current = Average o/p current

$$= -\frac{16.878}{8} = -2.10A$$

 




# Single Phase Full-wave AC

 
## Regulator / Controller

Caution: Gate ckt for two thyrs need to be isolated!



Vav is:
 
$$V_{av} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t)$$




(or)

$$V_{av} = \frac{V_m}{\pi} \left[ -\cos \omega t \right]_{\alpha}^{\pi}$$


 
$$V_{av} = \frac{V_m}{\pi} (1 + \cos \alpha) \dots (6.4)$$



Rms of p voltage:

$$V_L = \left[ \frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t) \right]^{0.5}$$



$$= \frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) \, d(\omega t)$$

(or)

$$V_L = V_m \left[ \frac{1}{2\pi} \left( \pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right] \dots (6.5)$$

# Single Phase Full-wave AC Controller

## Some more Configurations

\* Gate circuits need not to be isolated. During +ve h.cycle TH1 and D1 conducts, during -ve h.cycle TH2 and D2 conducts. Power consumption of this ckt is higher than previous case.

TRAC

(Page 82)



Diagram diagrams

\* After every alternate cycle TRIAC is to triggered again.

  
## Single $\phi$ Full-wave AC Controllers R-L Load

P-32


\* If both thyristors are connected firing angle is same for them in case both are triggered same time this is reduced in this ckt



(Single  $\phi$  regulator using TRIAC)

 

### 3 $\phi$ Full-wave AC Regulators

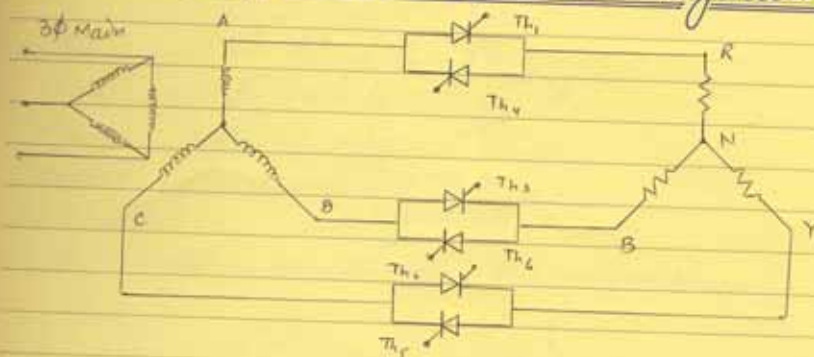

$$* V_L = \sqrt{3} V_m \left[ \frac{1}{\pi} \left( \frac{5\pi - \alpha}{24} + \frac{\sin 2\alpha}{4} + \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{0.5}$$

### 3- $\phi$ Full-wave AC Controllers

#### Other possible Connections

##### Tie Connection:

- \* Neutral is connected with control circuit.
- \* Load is on star and supply is delta.

Date 03, 04, 2008

Delta connections:

\* This connection used where no possibility to change type of system means the star is available.

\*  $\alpha$  should be same  $\forall$  phases.

## CYCLOCONVERTERS

\* Essentially a frequency converter.

\* A single step process in dc we don't convert AC - DC then again AC.

\* Converters / regulators convert fixed AC into variable or fixed AC output voltage but frequency remains the same.

\* A cyclo-converter gives variable AC voltage with diff frequency!

\* One way of accomplishing is a two step operation, first conversion of AC - DC then converting DC into diff freq AC thru inversion!

\* By using a cycloconverter this 2 step process can be avoided and made more simple!

\* A cycloconverter converts AC of one freq into other without involving DC conversion processes.

Date 03, 04, 2008

Delta connections:

\* This connection used where no possibility to change type of system means the star is available.

\*  $\alpha$  should be same  $\forall$  phases.

## CYCLOCONVERTERS

\* Essentially a frequency converter.

\* A single step process in dc we don't convert AC - DC then again AC.

\* Converters / regulators convert fixed AC into variable or fixed AC output voltage but frequency remains the same.

\* A cyclo-converter gives variable AC voltage with diff frequency!

\* One way of accomplishing is a two step operation, first conversion of AC - DC then converting DC into diff freq AC thru inversion!

\* By using a cycloconverter this 2 step process can be avoided and made more simple!

\* A cycloconverter converts AC of one freq into other without involving DC conversion processes.

Date 03.04.2008

\* Hence its an AC-AC converter with diff freq without any intermediate DC link.


Types:

- (1) Single  $\phi$  to Single  $\phi$
- (2) 3 $\phi$  to single  $\phi$
- (3) 3 $\phi$  to 3 $\phi$

- \* These can be step up or down.
- \* Step up would mean o/p freq is higher than i/p.
- \* Step down vice versa.
- \* " " uses natural or line commutation whereas step up uses forced commutation.
- \* They were initially developed for electrical traction. (conveyor belt, electric locomotive)  
 (Physical movement of heavy load using electrical energy)




Principle of operation

Date

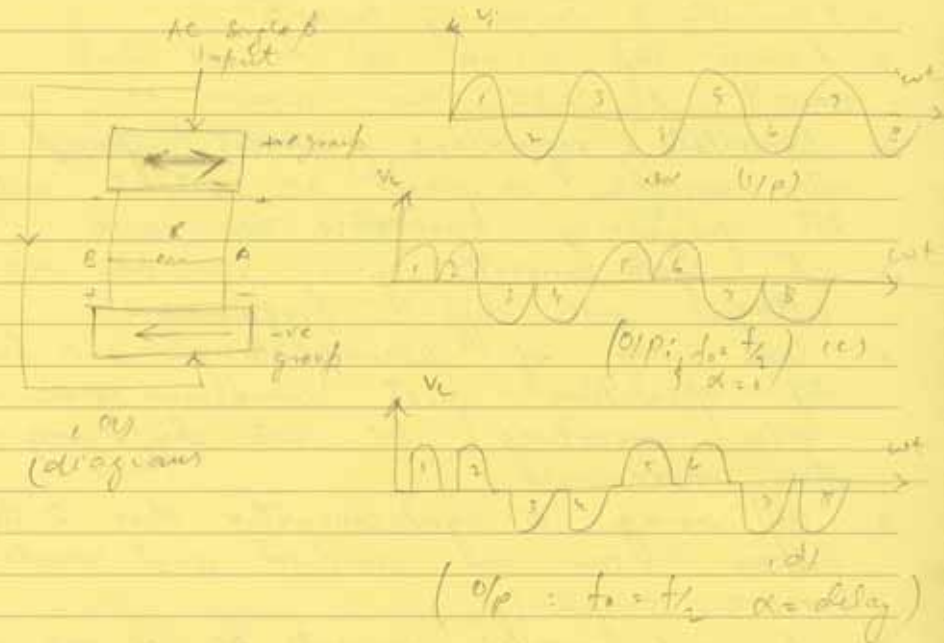

# Single $\phi$ cycloconverter Centre Tapped

Date

   

| No of half cycle $1/2$ | Thyr $T_{1/2}$ | Path of $I$              | Direction of $I$ thru load |
|------------------------|----------------|--------------------------|----------------------------|
| 1                      | $T_{11}$       | A - $T_{11}$ - C - O - A | C to O                     |
| 2                      | $T_{22}$       | B - $T_{22}$ - C - O - B | C to O                     |
| 3                      | $T_{11}$       | A - $T_{11}$ - C - O - A | C to O                     |
| 4                      | $T_{23}$       | O - C - $T_{23}$ - O     | O to C                     |
| 5                      | $T_{14}$       | O - C - $T_{14}$ - O     | O to C                     |
| 6                      | $T_{23}$       | O - C - $T_{23}$ - O     | O to C                     |

Date 03.04.2008

## INVERTERS


- \* It's a dc to ac converter.
- \* The  $\omega$  voltage and freq can be varied as per requirement of load.
- \*  $V_p$  may be from a battery, a solar cell or fuel cell.
- \* Utilization:
  - o Domestic application.
  - o Commercial installation as a source of steady power.
  - o variable speed ac drives.
  - o Induction heating.
  - o HVDC power transmission.

## Classification


- \* With respect to:
  - (1) Single or 3  $\phi$
  - (2) Naturally commutated or forced commutated.
  - (3) The connections of thyr viz: series, parallel or bridge.

Date 03.04.2008

# Series Inverter

 

(a)

 

## Modes of Operation

- Mode 1:  $Th_1$  ON.
- Mode 2:  $Th_1$  &  $Th_2$  both OFF.
- Mode 3:  $Th_2$  ON.

\* Series inv is so called due to commutating elements in series with load.

\* Due to LC tank cap is charged at  $V+Ec$  and continues to charge in opposite polarity.

$$R^2 < 4L/C$$

\* Drawbacks: ckt can't operated without Mode 2. Can't turn ON both SCR's at a time.

Date 03.04.2008

The above sequence is modes is repeated in next cycle when  $Th_1$  is turned ON. The freq of o/p voltage is:

$$f = \left[ \frac{1}{2\left(\frac{T}{2} + T_{off}\right)} \right] \text{ Hz} \quad \dots (4.2)$$

where,  $\frac{T}{2}$  = Time period of oscillation and  $T_{off}$  is time gap b/w turn off one thyx and turn ON of 2nd thyx.

Also,

$$\frac{T}{2} = \frac{\pi}{\left(\frac{1}{LC} - \frac{R^2}{4L^2}\right)^{0.5}} = \frac{\pi}{\omega_r} \quad \dots (4.3)$$

(b) Analysis:

When  $Th_1$  is turned ON, KVL

$$V + E_c = Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

where

$E_c$  is initial voltage across cap.

Taking Laplace transform:

$$\frac{V}{s} + \frac{E_c}{s} = I(s) \left[ R + sL + \frac{1}{Cs} \right] \quad \dots (4.5)$$

Since ckt is underdamped solution for (4.5) is

$$i = \frac{V + E_c}{\omega_r L} e^{-\frac{Rt}{2L}} \sin(\omega_r t) \quad \dots (4.6)$$

where


$$\omega_r = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \quad (\text{rad})$$

### Drawbacks

1. - The max possible freq is limited to damped freq of  $\omega_{cn}$  i.e  $\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$ . This is due to fact that  $Th_1$  must be turned off before  $Th_2$  is turned ON otherwise the supply voltage 'V' will be short cktd.
2. - When freq is less than damped freq distortion of op voltage waveform is high b/c  $T_{off}$  is large in comparison with ON time.
3. - The ckt component carry load I continuously. The cap supplies load I in every -ve h/c. Thus 'I' rating of commutating elements L and C are high.
4. - The source supplies load intermittently (only during +ve h/c). Therefore, source should have a high 'I' rating also. Source current has high Harmonic content.
5. - Max load 'I' current depends on load resistance. Therefore output regulation of inverter is poor.

 
### Modified Series Inverter

\* Problem is removed but cost of extra power ~~conv~~ consumption.



### Parallel Inverter

Day

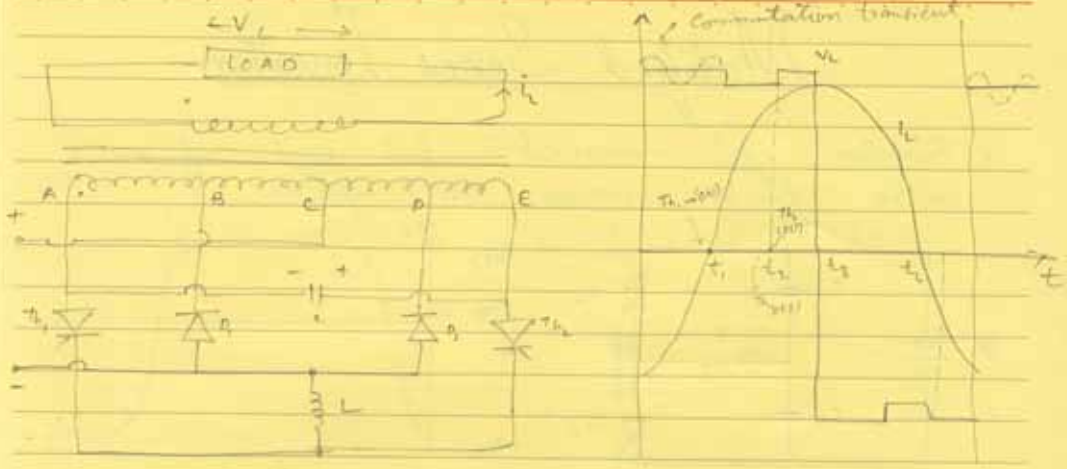

(Parallel Inverter)

(PARALLEL Inverter)

Cap and load are effectively in parallel.

MODE 1:

- Th<sub>1</sub> turned ON at t<sub>1</sub>.
- Battery current flows thru C-A-Th<sub>1</sub>-L.
- No. of turns CA EC and secondary are equal. Thus voltage b/w E & A is 2V (if V is up to II-inverter).
- Due to 'L' nature of load, load current inc gradually.

MODE 2:

- Th<sub>2</sub> is ON at t<sub>2</sub>.
- C turns Th<sub>1</sub> OFF.
- Current flows: Th<sub>2</sub> - L - D<sub>1</sub> - B - A
- Load voltage will be +ve and more than battery voltage.
- I<sub>L</sub> will flow thru CB and diode D<sub>1</sub> to -ve of battery bc D<sub>1</sub> is fwd bias and cap discharge current is more than load current.
- Potential at B raises sufficiently to rev bias D<sub>1</sub>.
- The Cap discharge thru Th<sub>2</sub> will stop.
- Now inductor current will take path: L - D<sub>2</sub> - DE - Th<sub>2</sub> will during this D is connected to -ve of battery hence polarity of VL will rev and cap will be charged to slightly more than 2V now in opposite direction.



Date 09.04.2008

- $T_{h1}$  will stop when  $i_L$  current becomes zero thru it.

### MODE 3:

- when  $i_L$  will = 0,  $D_2$  stops conducting.
- Then at  $t_4$  the  $T_{h1}$  is triggered ON again to reverse the direction of current thru load.
- During  $t_4$  to  $t_5$  load voltage  $V_L$  and load current  $i_L$  are reversed.
- At  $t_5$ ,  $T_{h1}$  is triggered ON again.

### Some Observations:

- Each of thyr turns ON twice during each half cycle.
- Interval  $t_2$  to  $t_4$  is load dependant.
- Thus each thyr has to be gated by a pulse train for a minimum duration of  $\frac{1}{4}$  cycle.
- Feedback diode conducts during  $t_2$  to  $t_4$ , and during this period load voltage will be more than  $V$ .

### Control of output Voltage

- The op voltage can be controlled from dc side or from ac side.
- In control from dc side, 1/p dc

Date 10.4.08

voltage is varied and this changes op rms voltage.

- + Variable 1/p voltage can be obtained either from a controlled rectifier or from a chopper circuit.
- + Chopper circuit introduces greater harmonics thru.
- \* Control from ac side would include a transformer mostly with multiple tapping.

### Design of Commutation elements 'L' & 'C':

The diode  $D_1$  will conduct till current reaches peak value. when  $D_1$  conducts,  $T_{h1}$  is reverse biased this time must be allowed equal to turn off time of SCR.

$$t_q = \frac{1}{3} \sqrt{LC}$$

Also reflected load current at secondary of trfr is given by

$$i_L = V \sqrt{\frac{C}{L}}$$

Example 4.4: A parallel inverter has i/p dc voltage of 40V. It is desired that o/p voltage to be 230V, 50Hz and peak load current 2A. Design parallel inverter, chose correct ratings of scr

if

let Turn off time = 50 μsec  
load current  $i_L = 2A$

Since i/p is 40V & o/p is 230V

Reflected load current is given by

$$i_L' \times 40 = 2 \times 230$$

$$i_L' = \frac{460}{40}$$

$$i_L' = 11.5 A$$

Now using eq 4.10 & 4.11

$$t_q = \frac{\pi}{3} \sqrt{LC}$$

$$50 \times 10^{-6} = \frac{\pi}{3} \sqrt{LC}$$

$$\frac{\pi}{9} LC = 50 \times 10^{-12}$$

And

$$i_L = V \sqrt{\frac{C}{L}}$$

So

$$L = 166.04 \mu H$$

$$C = 13.73 \mu F$$



The reflected load current is 11.5A, allowing a margin of about 1.5, SCR current rating is 20A. Voltage rating of 100V is suitable.

Therefore, a voltage rating of 100V is suitable with 20A of current and 50 μsec to turn-off time.

# Power Electronics

## PWM Techniques

They come under fundamental techniques.

  

\* o/p generated depending upon decision taken in waveform-1

\* If in waveform-1 reference voltage is inc<sup>t</sup> the o/p pulse width will change.

o The rms value of voltage is

$$V_L = \left[ \frac{2}{2\pi} \int_{\frac{\pi-\delta}{2}}^{\frac{\pi+\delta}{2}} v^2 dt \right]^{0.5} = V \sqrt{\frac{\delta}{\pi}} \quad (4.16)$$

where V is 1/π voltage.

The fourier series of voltage is

$$V_L(t) = \sum_{n=1,3,5}^{\infty} \frac{4V}{n\pi} \frac{\sin n\delta}{2} \sin(n\omega t) \quad (4.17)$$



o The even harmonics are absent in waveform as it is symmetrical waveform. □ resulted.

## Multiple PWM

\* Single PWM technique has higher harmonic content in o/p waveform.

\* The harmonic content can be reduced by having many pulses in each half cycle of o/p

  \* If higher harmonics lower the fundamental content. (10)



The freq of reference signal  $A_r$  control frequency of o/p. The carrier signal is a triangular wave having a frequency ( $f_c$ ). Freq ( $f_c$ ) determines number of pulses in each half cycle. The ratio  $f_c$  is known frequency modulation ratio ( $f_m \Rightarrow$  freq of o/p). The no. of pulses in each h. cycle is:

$$p = \frac{f_c}{2f_o} = \frac{m_f}{2} \quad (4.18)$$



where 'p'  $\Rightarrow$  no. of pulse in each h.c. and  $m_f \Rightarrow$  modulation ratio.

$\Rightarrow$  The variation of ratio  $\left(\frac{A_r}{A_c}\right)$  0 to 1 changes pulse width from 0 to  $\frac{\pi}{p}$  and o/p voltage from 0 to V. P width of each pulse the rms value of o/p is:

$$V_L = \left[ \frac{2P}{2\pi} \int_{\frac{\pi}{p} - \frac{\delta}{2}}^{\frac{\pi}{p} + \frac{\delta}{2}} V^2 d(\omega t) \right]^{0.5}$$

$$V_L = V \sqrt{\frac{p\delta}{\pi}} \quad (4.19)$$

Sinusoidal PWM

  

Extract info from web on HV high voltage DC transmission, the report would be based on operational methods, merits and limitation. The report will be in own words should not exceed 4-44 pages (2 pages-back to back). All diagrams / sketches for explanation would be drawn in freehand. (Next Wednesday) (Assignment # 2)

(in PWM)

- \* The reference signal is a sinusoidal wave.
- \* The control sig is a triangular wave frequency  $f_c$ .
- \* Sinusoidal sig's frequency controls frequency of o/p voltage of inverter.
- \* The peak value  $A_r$  of reference sig controls modulation index.
- \* The carrier and reference waves are mixed in a comparator.
- \* When magnitude of reference signal is more than that of carrier signal then o/p of comparator is high and pulse is generated.
- \* This pulse triggers SCR into conduction and a voltage o/p occurs.

(103)

- \* The widths of  $n$  pulses are not same.
- \* Width depends upon angular position of pulse.
- \* Pulse width is direct  $\propto$  angle.
- \* By varying modulation index, we can vary rms value of o/p waveform.
- \* If  $\delta_m$  width of  $m$ th pulse the rms value of o/p voltage is

$$V_L = V \left[ \sum_{m=1}^p \frac{\delta_m}{\pi} \right]^{0.5} \quad (4.20)$$

where 'p' is no. of pulses on one cycle of o/p waveform.

(Example: 4.13) A single  $\phi$  full bridge inverter has purely resistive load and its voltage is controlled by multiple pulse width modulation technique.

The width of each pulse is  $30^\circ$  and each cycle has 5 pulses. If voltage 200V. find (a) rms value of o/p.

(b) pulse width to maintain o/p power constant if i/p voltage inc by 10%

(c) Maximum possible i/p voltage if max possible pulse is  $33^\circ$ .

(104)

(17,04,08)

4.13

88  
82

(a)  $V_L = 200 \sqrt{\frac{5 \times 30}{180}}$

$V_L = 182.57 \text{ V}$

(b) Input voltage =  $200 \times 10\% = 20$   
 $= 220 \text{ V}$

$182.57 = 220 \sqrt{\frac{5 \times \delta}{180}}$

$\sqrt{\frac{5 \times \delta}{180}} = \frac{182.57}{220}$

$\frac{5 \times \delta}{180} = (0.8298)^2$

$\frac{5 \times \delta}{180} = 0.6886$

$\delta = 24.79^\circ$

(c)  $182.57 = V \sqrt{\frac{5 \times 33}{180}}$

$V = 190.65 \text{ V}$



(Ex: 4.14) A single  $\phi$  full-bridge inverter is fed by 200V DC source. The o/p voltage is controlled single PWM. The reference signal is more than for  $120^\circ$  in each half cycle. Find rms value of o/p?

88

with  $\delta = 120^\circ$   
eq (4.16)

$V_L = 200 \sqrt{\frac{120}{180}}$

$V_L = 163.3 \text{ V}$

(Ex: 4.15) A single  $\phi$  inverter is controlled by sinusoidal PWM. The i/p volts is 150. The ref and control sigs are so adjust that ref signal is more than signal from  $20^\circ$  to  $40^\circ$ ,  $60^\circ - 120^\circ$ ,  $140^\circ - 160^\circ$  in each half cycle. Find rms o/p

88

There are 3 pulses in each cycle. The width of first pulse  $20^\circ$ , 2nd =  $3^{\text{rd}} = 20^\circ$

using eq (4.20)

$V_L = 150 \left[ \frac{20}{180} + \frac{60}{180} + \frac{20}{180} \right]^{0.5}$

$V_L = 111.80 \text{ V}$





(17,04,08)
 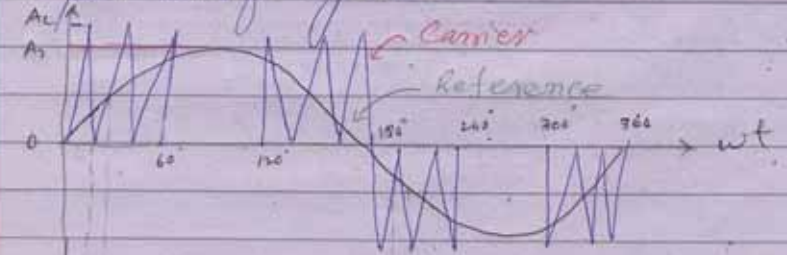
# Modified PWM

(slide 10)

- \* The width of pulse near peak of sine wave does not vary with variation of modn index.
- \* This is due to property of sine wave and based upon it sinusoidal PWM technique can be modified.
- \* In modified sinusoidal pulse w.m. (MSPWM) technique, carrier wave is applied during fast and fast 60° intervals per half cycle.




Draw up below here ↓

- \* Advantages of this technique:
  - ⊕ Fundamental component is inc ↑ and its harmonic characteristics are improved.
  - ⊕ It reduces no. of switching of power devices and also reduces switching losses.

## Advanced modulation Techniques

- \* The sinusoidal pulse w. mod tech. suffers from draw back of lower fundamental level.
- \* The following are other modulation techniques that offers improved performance:
  - (1) Trapezoidal.
  - (2) Staircase.
  - (3) Stepped.
  - (4) Harmonic injection.
  - (5) Delta modulation.

# (1) Trapezoidal Modulation

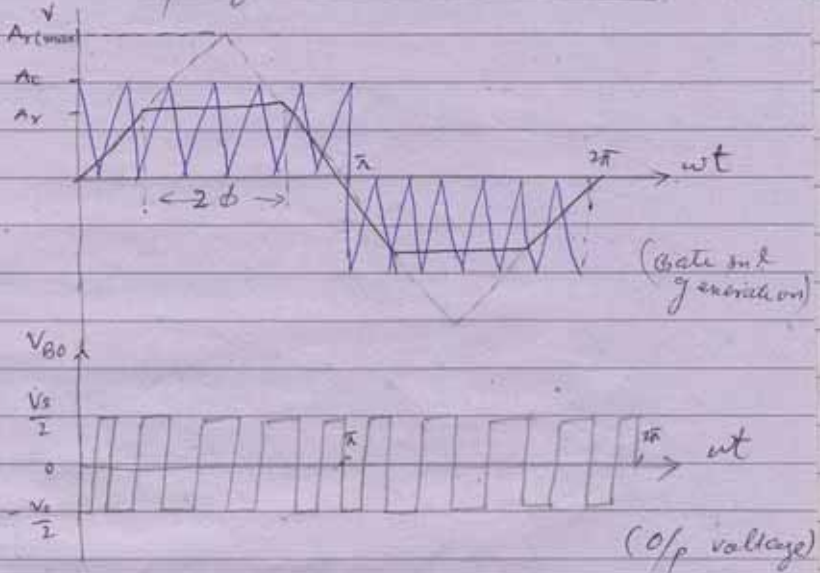

- \* A triangular wave is compared with a modulating trapezoidal wave.
- \* The trapezoidal wave can be obtained from triangular wave by limiting its magnitude to  $\pm A_r$ , etc. It is related to peak value  $A_r(\text{max})$  by

$$A_r = \delta A_r(\text{max})$$

where 's' is called triangular factor, i.e. waveform becomes a  $\Delta$  wave

when  $\delta = 1$ , the mod index  $M$  is

$$M = \frac{A_r}{A_c} = \delta \frac{A_r(\text{max})}{A_c}$$

for  $0.5 \leq \delta \leq 1$  (6.48)

\* The angle of flat portion of trapezoidal wave is given by:



$$2\phi = (1 - \delta)\pi \quad (6.49)$$

\* For fixed values of  $A_r(\text{max})$  and  $A_c$ ,  $M$  that varies with o/p voltage can be varied by changing triangular factor ( $\delta$ ). This type of mod'n inc peak for fundamental o/p voltage up to 1.05  $V_s$ , but o/p contain Lower order harmonics (LOHs).


  
## (2) Stair Case Modulation

In this technique you can pick a specific harmonic point and change variate it according to requirement.



The stair case is not a sampled approximation to sine wave rather the levels of stair are calculated to eliminate certain harmonics.

The modn freq ( $m_f$ ), and no. of steps are chosen to obtain desired



quality of s/p voltage

+ Not recommended for fewer than pulses in 1 cycle.

+ with this method high quality having fundamental value of upto 0.94 V<sub>s</sub> can be achieved.

23, 04, 08

## (3) Stepped Modulation

 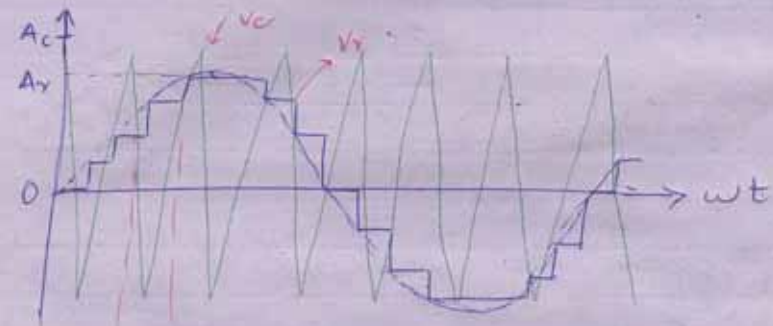

+ Uniform steps.

+ Not approximation of sine wave

(23,04,08)



- \* Modulating signal is stepped wave as shown in figure.
- \* It is not a sampled approximation to the sine wave rather it is divided into steps say  $20^\circ$  with each interval.
- \* This controls specific harmonic contents to control specific harmonic contents to control fundamental and even can eliminate certain harmonics.
- \* Such type of PWM gives higher fundamental amplitude with low distortion.

Control elements:

- (1) No. of pulse.
- (2) Step length
- (3) Step height.

⊙ to control fundamental, to suppress power of harmonics, to target specific harmonic content.

## (14) Harmonic Injection Modulation

  

- \* The modulating signal is generated by injecting selected harmonics to sine wave.
- \* As a result of that, a flat-topped waveform is generated which reduces amount of over-modulation.
- \* It provides a higher fundamental amplitude with lesser distortion.

\* Generally modulating signal is composed of:

(6.50)  $v_g = 1.15 \sin \omega t + 0.27 \sin 3\omega t - 0.029 \sin 9\omega t$


\* Injection of 3<sup>rd</sup> harmonic does not affect quality of output voltage, 6% of a 3 $\phi$  inverter does not contain triplen harmonics.

\* If only 3<sup>rd</sup> harmonic is injected the modulating signal is given by

and  $v_g = 1.15 \sin \omega t + 0.19 \sin 3\omega t$

\* The signal can be generated (6.51) by  $\frac{2\pi}{3}$  segments of a sine wave as shown.

 Q Draw the modulating signal waveform for a harmonic injection modulation when freq of fundamental is 50Hz?





Features of this PWM:

- \* The line to line voltage is sinusoidal form and amplitude of fundamental component is approximately 15% more than that of a normal sinusoidal pw
- \* As obvious, each arm is switched off for 1/3<sup>rd</sup> of period, heating of switching devices is reduced.

124, 04


(5) Delta Modulation

  

24.04.08

\* Base of delta modulation  $\rightarrow$

\* Specialized triangular wave form

 

\* A triangular <sup>wave</sup> is allowed to oscillate within a defined window  $\Delta V$  above and below reference sine wave  $V_r$ .

\* The modulation is also called hysteresis modulation.

\* Change in modulating and freq (keeping slope of  $\Delta$  wave constant) would result in change in the pulse width and no. of pulses.

Hysteresis: Quality of a system to obtain its original position.

Depends on amount of current, and core material.

\* If hysteresis of inverter is large, inverter is lorry.

\* To change off simply change frequency of carrier signal!

\* The fundamental of voltage can be upto  $1V_s$  and is dependent on peak amplitude  $A_r$  and freq  $f_r$  of reference signal.

\* The delta modn. can control ratio voltage to freq, which is utilized in ac motor speed control.

(24.04.08)


## Voltage Control of 3 $\phi$ Converter

\* A 3 $\phi$  inverter can be thought as <sup>3 sin</sup> 3 $\phi$  converters operating in parallel.

\* With this analogy, all previous techs can be utilized to control of voltage of 3 $\phi$  Converter, however following are most common techniques for of voltage control of 3 $\phi$  converter.

- 1- Sinusoidal PWM.
- 2- 3<sup>rd</sup> Harmonic PWM.
- 3- 60° PWM.


1- Sinusoidal PWM (3.19)

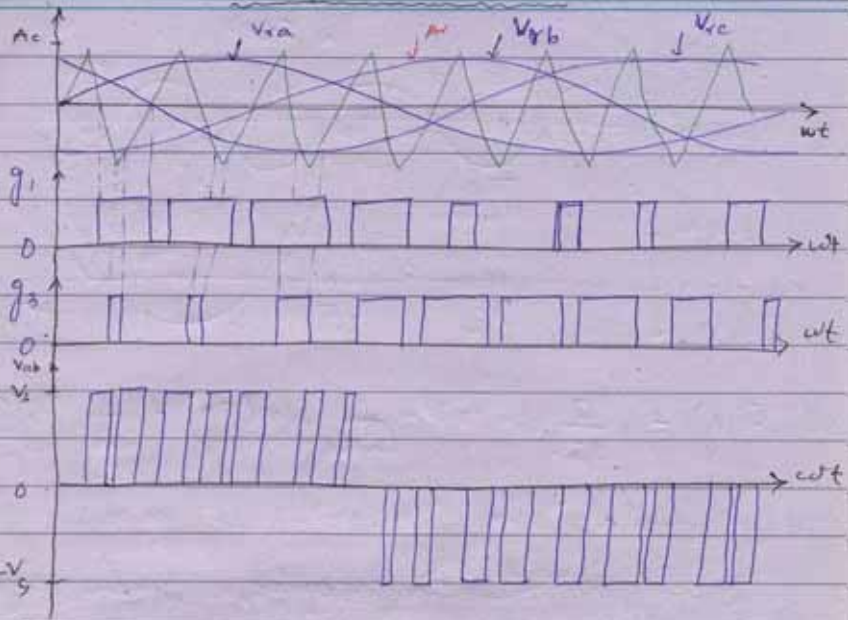

The peak amplitude of line to line voltage is given by


$$V_{ab,1} = M \sqrt{3} V_s / 2 \quad \text{for } 0 \leq M \leq 1$$

2- 60° PWM (3.20)

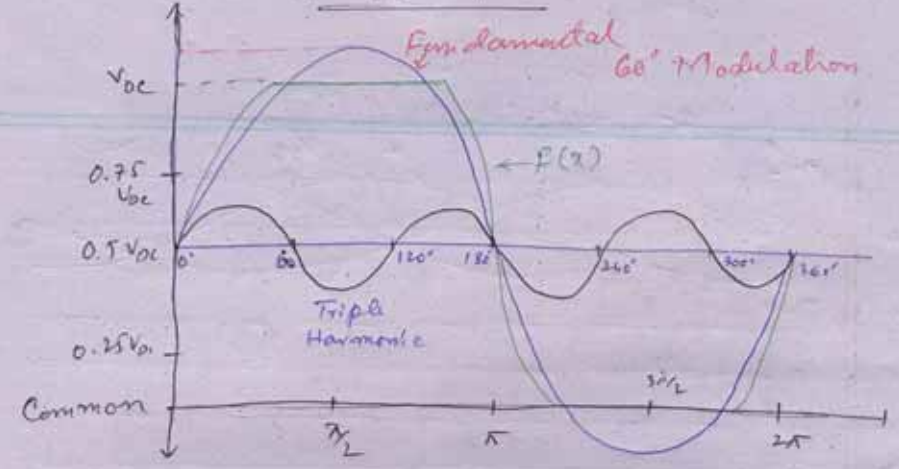

$$F(x) = \frac{2}{\sqrt{3}} \sin(x) + \frac{1}{2\pi} \sin(3x) + \frac{1}{60\pi} \sin(9x) + \frac{1}{200\pi} \dots$$

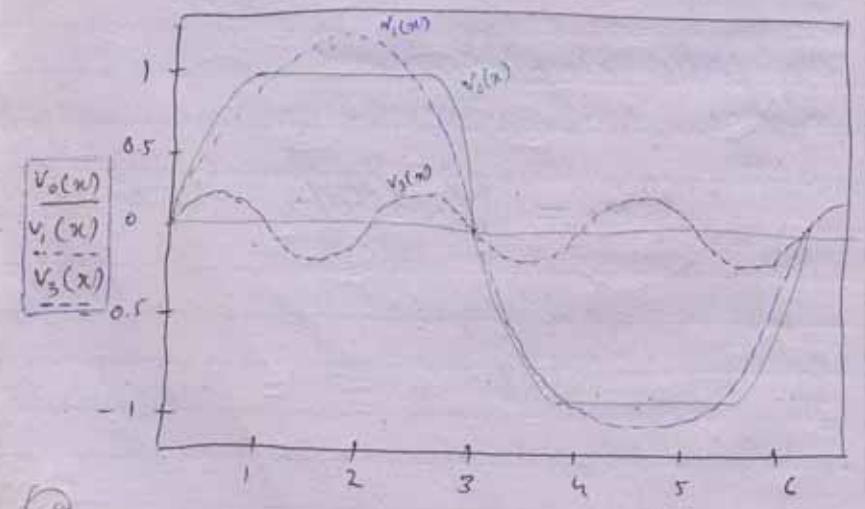∴ modulating signal contains fundamental and 3rd harmonic component only



(24-04-08)  
(p. 24)

2-60° PWM?

\* 60° PWM is similar to modified PWM

\* The idea is to make modulating signal flat top from 60° to 120° and then from 240° to 300°.

\* The power devices are held on for one-third of cycle and thus have reduced switching losses.

\* All triple harmonics are absent in 3φ voltages.

\* 60° PWM creates a larger fundamental & utilizes more of available DC voltage.

\* Phase voltage:  $V_p = \frac{0.57735}{V_s}$

and line voltage:  $V_L = V_s$

2 Draw the wave form of modulating signal for a 3φ, 60° PWM system operating at a fundamental freq of 50 Hz?

$f = 50 \text{ Hz}$

$f(0^\circ) = 0, f(30^\circ) = 71.24, f(60^\circ) = 1, f(90^\circ) = -69.51$   
 $f(120^\circ) = 1, f(150^\circ) = 71.24, f(180^\circ) = 0, f(210^\circ) = -71.24$


$f(240^\circ) = -1, f(270^\circ) = -69.51$

$f(300^\circ) = -1, f(330^\circ) = -71.24$

$f(360^\circ) = 0$


$f(0^\circ) = 0, 0.731, 1, 1, 0.731, 0, -0.731, -1, -0.731, 0$

(3) 3φ Harmonic PWM

 

$F(x) = \frac{2}{\sqrt{3}} \sin(x) + \frac{1}{3\sqrt{3}} \sin(3x)$

26/04/00

 

- \* 5<sup>th</sup> harmonic PWM is similar to selected harmonic injection method.
- \* The diff is that reference ac waveform is not sinusoidal but consist of both a fundamental component and a 3<sup>rd</sup> harmonic component.
- \* As a result peak-peak amplitude of ref fms does not exceed DC supply  $V_s$ .
- \* But fundamental component is higher than supply.
- \* 3<sup>rd</sup> harmonics are cancelled out in motor neutral as before.
- \*  $V_p = V_s / \sqrt{3} = 0.57735 V_s$

\* The fundamental component peak amplitude  $V_{p1} = 0.57735 V_s$  and peak voltage is  $V_L = \sqrt{3} V_p = \sqrt{3} (0.57735 V_s)$

∴  $V_L = V_s$

\* This is 15.5% higher in amplitude than sinusoidal PWM.

## DC-DC CONVERTER (CHOPPER)

02, 05

- \* Industrial applications often require fixed DC voltage to be converted into variable DC voltage.
- \* DC-DC converter performs that operation.
- \* It is equivalent to  $\frac{1}{2}$  in AC.
- \* Buck and Boost operations are possible.
 



|                    |   |
|--------------------|---|
| * Buck - step down | Buck-boost<br>↳ Variable<br>step down or up |
| * Boost - step up  |   |

02, 05, 08

- \* Typical Applications include:
- \* Traction motor control in electric trolley, automobile, marine, hoists, forklift, track and mine haulers.
- \* Properties: Smooth acceleration control high  $\eta$  and fast dynamic response.
- \* They can be used in regenerative braking of DC motor.
- \* This returns back energy to supply and this saves energy for transportation system for frequent stops. e.g. Automobile industry: train halt.
- \* DC convts are used in voltage regulators with inductor to make constant current source.


### Step down DC-DC Converter (7)

02,

 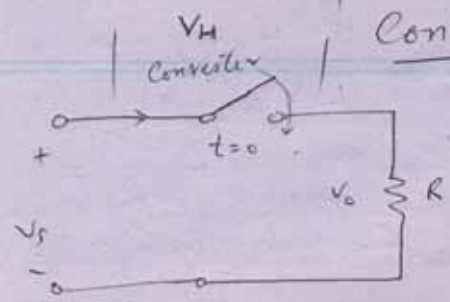

S.1 (a)

Very very basic type of buck converter.

 

\* As there is turn-off time is present so  $A_{v} < 1$  (Basic theory)

\*  $V_H$  := voltage drop of switching device.

\* The average o/p is given by

$$V_a = \frac{1}{T} \int_0^{t_1} V_o dt = \frac{t_1}{T} V_s = f t_1 V_s$$

$$V_a = k V_s$$

and average load current

$$I_a = V_a / R = k V_s / R$$



(02,05,03)

and avg load  
where

'T' is chopping period

'k' =  $t_1/T$  is duty cycle  
chopper

'f' is chopping frequency.

Rms value of o/p is

$$V_o = \left( \frac{1}{T} \int_0^{kT} v_o^2 dt \right)^{1/2}$$

$$V_o = \sqrt{k} V_s \quad (5.2)$$

Assuming a lossless converter,  
i/p power to converter is as  
o/p power and given by:

$$P_i = \frac{1}{T} \int_0^{kT} v_i i dt = \frac{1}{T} \int_0^{kT} \frac{v_o^2}{R} dt$$

$$P_i = k \frac{V_s^2}{R} \quad (5.3)$$

Effective i/p resistance seen  
by same source is;

$$R_i = \frac{V_s}{I_a} = \frac{V_s}{kV_s/R} = \frac{R}{k} \quad (5.4)$$

\* This means that converter makes  
i/p resistance  $R_i$  as a variable  
resistance  $R/k$ .

\* i/p resistance is  $\propto$  of duty  
cycle.

$$R_i = \frac{R}{k} = \frac{R}{t_1/T} \quad (10)$$

\* Duty cycle 'k' can varied by:  
 $\rightarrow$  varying  $t_1$ , T or f.

\* o/p voltage thus can be varied  
from 0 to  $V_s$ .

\* Control freq. Operation:

f and thus T is kept constant,  
the ON time  $t_1$  is varied,  
Pwidth thus varies, this called  
PWM Control.

\* Variable freq. oper

(0.5, 0.5, 0.5)

Variable Freq Operations (ii)

Switching frequency  $f$  is varied, either on or off time is kept constant called FM large freq variation is required for complete control of o/p voltage.

This would generate harmonics at an predictable freq and filter design would be difficult.

Pinching Performances of a DC-DC converter (12)

The dc converter in fig 5.1a has  $R = 10 \Omega$  i/p voltage  $V_s = 220V$  when converter remains ON  $V_{CH} = 2V$  and chopping freq  $f = 1kHz$  duty cycle 50%. Determine (a) Avg o/p V (b)  $R_{ms}$  of  $V_o$  (c)  $\eta$  (d)  $R_i$  (e)  $R_{ms}$  of fundamental component of o/p harmonic voltage.

eg  $\Rightarrow$  (5.1)  $V_a = k V_s \Rightarrow 0.5 \times (220 - 2)$   
eg  $\Rightarrow$  (5.2)  $V_o = \sqrt{k} V_s \Rightarrow 50.5 \times (220 - 2) = 11015 V$

(c)

$$P_o = k \frac{(V_s - V_{CH})^2}{R} \quad \text{--- (5.5)}$$

$$= (0.5) \frac{(220 - 2)^2}{10}$$

$$P_o = 2376.2 W$$

$\times$  i/p can found from

$$P_i = k \frac{V_s (V_s - V_{CH})}{R} \quad \text{--- (5.6)}$$

$$= (0.5) \frac{(220)(220 - 2)}{10}$$

$$P_i = 2398 W$$

$$\eta = \frac{P_o}{P_i} = \frac{2376.2}{2398} = 99\%$$

(d)

$$\text{eg (5.4) } R_i = \frac{R}{k} = \frac{10}{0.5} = 20 \Omega$$

(e)

o/p voltage can express in Fourier series as

(130)

$$v_o(t) = kV_s + \frac{V_s}{n\pi} \sum_{n=1}^{\infty} \sin 2n\pi k \cos 2n\pi ft + \frac{V_s}{n\pi} \sum_{n=1}^{\infty} (1 - \cos 2n\pi k) \sin 2n\pi ft \quad (5.7)$$

The fundamental component ( $n=1$ ) o/p voltage can be eq (5.7)

$$v_1(t) = \frac{V_s}{\pi} \left[ \sin 2\pi k \cos 2\pi ft + (1 - \cos 2\pi k) \sin 2\pi ft \right] \quad (5.8)$$

$$= \frac{220 \times 2}{\pi} \sin(2\pi \times 1000t)$$



$$= 140.06 \sin(6283.2t)$$

and its rms  $V_1 = 140.06 / \sqrt{2}$

$$V_1 = 99.04 \text{ V}$$
  
## Duty Cycle Generation (02, 0)

\* By comparing a DC reference sml with a saw-tooth wave the duty cycle can be generated.



The reference sml is given by

$$V_r = \frac{V_r}{T} t \quad (5.9)$$

w/c must equal to carrier signal

$$V_{cr} = \frac{V_r}{T} kT$$

w/c give duty cycle k as

(32)


$$k = \frac{V_{cr}}{V_r} = M \quad (5.10)$$

M := modulation index.



(02,05,08)

\* By varying carrier s.d.  $V_c$  from  $0 \rightarrow V_c$ , duty cycle 'k' can be varied from 0 to 1.


 
Step Down Converter  
With R-L load (07,05,08)



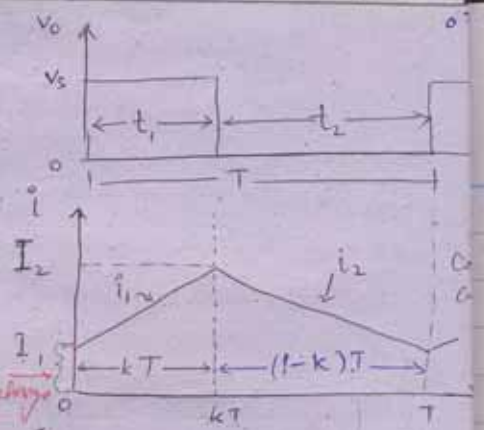 - \* Chopping is done by switch.
- \* Two modes of operation:
  - i) Close switch
  - ii) Open switch.
- \* Two mode of operation:
  - First mode: The converter is switched on, load current supplied thru supply.
  - 2nd mode: The converter is switched off, the load current is supplied thru free wheeling diode  $D_m$ .
- \* This would happen as shown:



L is not completely discharged

  


L is discharged


(a) Circuit

(b) Waveform

Step-up Operation

\* L-C Tank circuit

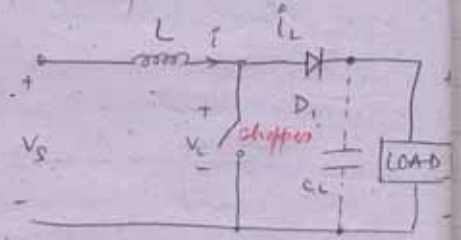

 

When converter is turned ON, voltage across 'L' is

$$v_L = L \frac{di}{dt}$$

and this gives p-p ripple current in 'L' as

$$\Delta I = \frac{V_s}{L} t_1 \quad (5.26)$$

The average current is

$$V_o = V_s + L \frac{\Delta I}{t_2} = V_s \left(1 + \frac{t_1}{t_2}\right)$$

$$V_o = V_s \frac{1}{1-k} \quad (5.27)$$



Connecting a cap at off (or slow) would make off continuous and  $V_o$  would become average value  $V_a$ .

As obvious from equation 5.27 we can vary off voltage and step it up, it by varying value of 'k'.

A Min off voltage is  $V_s$  when duty cycle ( $k=0$ ).

Making 'k' close to 1 would result in a high off as shown in diagram.

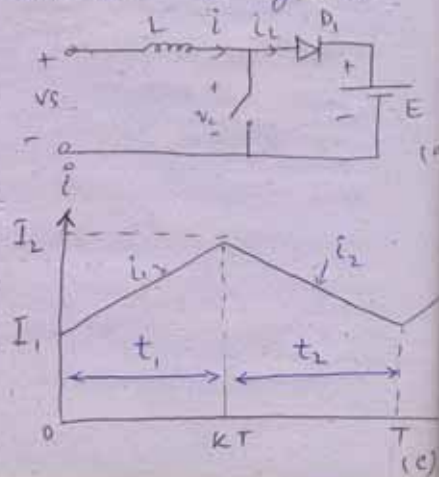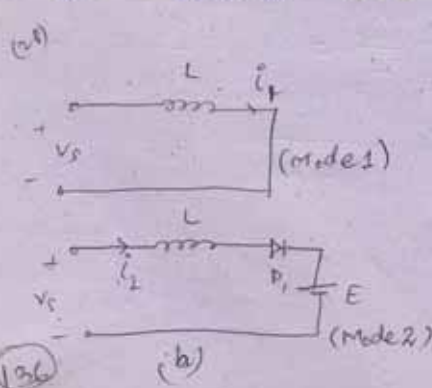This principle can be used to transfer energy from one source to other as shown below.



\*  $V_s < E$

- due presence of inductor
- low voltage source can transfer power to high voltage source

$V_s + V_L > E$

• E is absorbing power.

The inductor current for mode 1 is given by:

$V_s = L \frac{di}{dt}$

and expressed as

$i_1(t) = \frac{V_s}{L} t + I_1$  (5.28)

where  $I_1$  is initial current for mode 1.

During mode 1, current must rise and necessary condition

$\frac{di}{dt} > 0$  or  $V_s > 0$

The current for mode 2 is:

$V_s = L \frac{di_2}{dt} + E$

and solved as

$i_2(t) = \frac{V_s - E}{L} t + I_2$  (5)

where  $I_2$  is initial current for mode 2. For stable system current must fall and condition.

$\frac{di_2}{dt} < 0$  or  $V_s < E$

Stable systems A system free of oscillations

If condition is not satisfied, inductor current continues to rise and an unstable situation occurs.


Therefore, the condition for controllable power transfer as;

$0 < V_s < E$  (5.30)

Controllable power is only for stable systems.

For transferring power from a fixed (or variable) source to fixed dc voltage by (5.30) must be observed.

 In electrical braking of dc motors where motor behaves as a generator, the terminal voltage falls when machine's speed decr, converter permits power transfer to a fixed dc source or a rheostat.








When converter is turned on, energy is transferred from source  $V_s$  to inductor. If converter is off, a magnitude of energy stored in inductor is forced to battery  $E$ .

Without chopping action,  $V_s$  must be greater than  $E$  for transferring power from  $V_s$  to  $E$ .

     
# CONVERTER Classification

- \* Depending upon direction of current and voltage flow, dc converter can be classified to 5 type
  - o First Quadrant converter
  - o 2nd " "
  - o 1st & 2nd Quad "
  - o Third & 4th Quad "
  - o Four quadrant "




1st Quad Converter:

 The load current flows into load. Both  $V_L$  &  $I_L$  are +ve. This is rectifier mode of operation of converter.



2nd Quad Converter:

 
The  $I_L$  flows out of load. The load voltage is +ve but current is -ve. This is Inverter mode operation of converter.



1st and 2nd Quad:


$I_L$  is either +ve or -ve but  $V_L$  is always +ve. This type

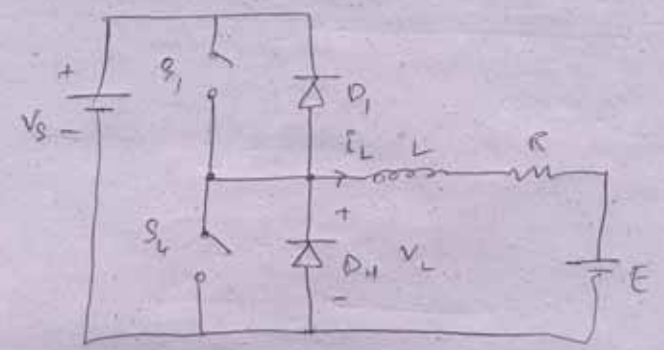of converter can either be operated as rectifier or an inverter.



3rd and 4th Quad:

 $I_L$  is either +ve or -ve but  $V_L$  is always -ve. Can be operated as rectifier or an inverter.




(Inverter mode)

(Rectifier mode)



 (13)

Four Quad Converter: This form basis of single  $\phi$  full bridge inverter- the  $V$  and  $I$  both can be +ve and -ve and a full control over power flow is available.



(#- bridge inverter)

|             |             |                    |                           |
|-------------|-------------|--------------------|---------------------------|
| $V_L + V_e$ | $i_L - V_e$ | $S_4$ (mod), $D_1$ | $S_1$ (modulating)        |
| $V_L - V_e$ | $i_L + V_e$ | $D_1, D_2$         | $S_2$ (continuous ON)     |
| $V_L + V_e$ | $i_L + V_e$ | $S_3$ (mod)        | $S_4$ (modulating), $D_3$ |
| $V_L - V_e$ | $i_L - V_e$ | $S_4$ (cont. ON)   | $D_3, D_4$                |
| $i_L - V_e$ | $i_L + V_e$ | $S_4, D_2$         |                           |

(a) Polarity


(b) Conducting devices

# Switching mode Regulators

- \* Chopper  $\rightarrow$  pulse width controlling.
- \* DC conv can be used as switching mode regulator to convert un-regulated DC to regulated DC.
- \* PWM technique at constant freq. is usually employed for that.
- \* Switching device maybe BJT, Mosfet or IGBT.
- \* Switching regs are commercially available in IC packages.
- \* The designer has to only choose external R & C value of oscillator reference.
- \* As a rule of thumb, to max  $\eta$  the min oscillator period should be about 100 times longer.

than transistor switching time.  
 If transistor has switching time of about 0.5  $\mu$ sec, the oscillator must oscillate at min period of 50  $\mu$ sec, w/c gives max oscillator freq of about 20kHz.

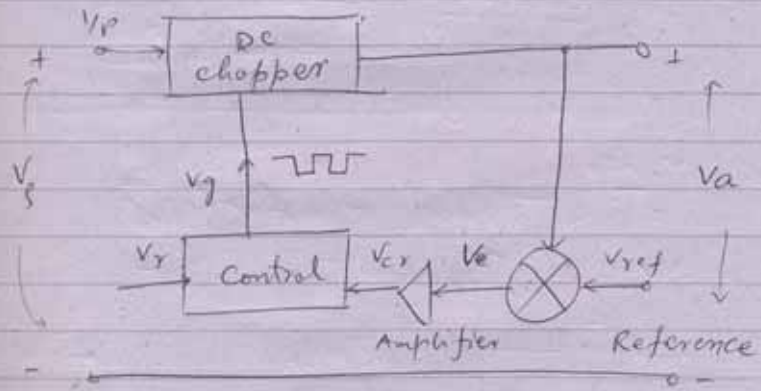A general switching mode regulator is shown below.




closed loop system.  
 +ve  $V_e$  (error voltage)  $\rightarrow$  pu

# Switching mode regulator Classification


1. Buck regulator
2. Boost reg
3. Buck-boost
4. Cuk reg.

## 1. Buck Regulator:

 


\* Modes:

- Trans conducting
- Trans not "

 


Mode (1)

 

Mode (2)

(147)

(Buck Regulator)

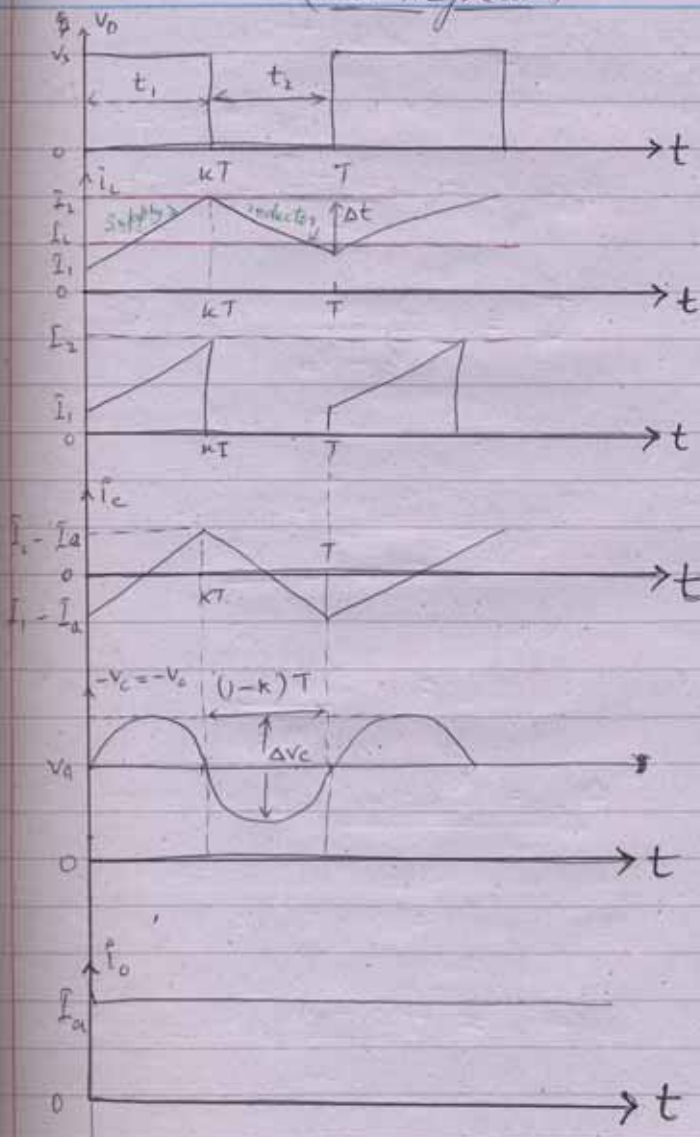

The voltage across 'L' is,

$$e_L = L \frac{di}{dt}$$

Assuming that inductor current rises linearly from  $I_1$  to  $I_2$  during time  $t_1$ 

$$V_s - V_a = L \frac{I_2 - I_1}{t_1} = L \frac{\Delta I}{t_1} \quad (5.44)$$

$$t_1 = \frac{\Delta I L}{V_s - V_a} \quad (5.45)$$

and inductor current falls linearly from  $I_2$  to  $I_1$  in time  $t_2$ :

$$-V_a = -L \frac{\Delta I}{t_2} \quad (5.46)$$

$$t_2 = \frac{\Delta I L}{V_a} \quad (5.47)$$

where  $\Delta I = I_2 - I_1$  is peak to peak ripple current of inductor. Equating value of  $\Delta I$  in Eqs. (5.44) & (5.46) we get

$$\Delta I = \frac{(V_s - V_a)t_1}{L} = \frac{V_a t_2}{L}$$

(148)

(32)

Substituting  $t_1 = kT$  and  $t_2 = (1-k)T$  yield average opp voltage ~~as~~

$$V_a = V_s \frac{t_1}{T} = k V_s \quad (5.48)$$

Assuming a lossless chit  
 $V_c I_c = V_a I_a = k V_s I_a$   
and 'p current (average)

$$I_s = k I_a \quad (5.49)$$

The switching period  $T$  can be expressed as

$$T = \frac{1}{f} = t_1 + t_2 = \frac{\Delta I L}{V_s - V_a} + \frac{\Delta I L}{V_a}$$

$$T = \frac{\Delta I L V_s}{V_a (V_s - V_a)} \quad (5.50)$$

we gives p-p ripple current as

$$\Delta I = \frac{V_a (V_s - V_a)}{f L V_s} \quad (5.51)$$

$$\Delta I = \frac{k V_s (1-k)}{f L} \quad (5.52)$$

By kirchoff's law of current we can write inductor current

$$i_L = i_c + i_o \quad (5.53)$$

if we assume that load ripple current  $\Delta i_o$  is very small and negligible  $\Delta i_L = \Delta i_c$  (5.54)

The avg cap current,  $i_c$  flows into for  $\frac{t_1}{2} + \frac{t_2}{2} = \frac{T}{2}$

$$I_c = \frac{\Delta I}{4}$$

the cap voltage is expressed as

$$V_c = \frac{1}{C} \int i_c dt + V_c(t=0)$$

peak-to-peak ripple ~~current~~ voltage of cap is

$$\Delta V_c = V_c - V_c(t=0) = \frac{1}{C} \int_0^{T/2} \frac{\Delta I}{4} dt = \frac{\Delta I T}{8C}$$
  
$$\Delta V_c = \frac{\Delta I}{8fC} \quad (5.55)$$

Substituting value of  $\Delta I$  from eq (5.51) or (5.52) in eq (5.53) yields

$$\Delta V_c = \frac{V_a(V_s - V_a)}{8LCf^2 V_s} \quad (5.54)$$

$$\Delta V_c = \frac{V_s k(1-k)}{8LCf^2} \quad (5.55)$$

Conditions for continuous L current and capacitor voltage:

If  $I_L$  is average inductor current, inductor ripple current  $\Delta I = 2I_L$

using eqs (5.48) and (5.52), we get

$$\Delta I = I_L - (-I_L) = 2I_L$$
$$\frac{V_s(1-k)k}{fL} = 2I_L = 2I_o = \frac{2kV_c}{R}$$

we gives critical value of inductor  $L_c$  as

$$L_c = L = \frac{(1-k)R}{2f} \quad (5.56)$$

If  $V_c$  is avg cap voltage, cap ripple voltage we get

$$\Delta V_c = 2V_a \text{ using (5.48) } \frac{1}{2} I_o$$
$$\Delta V_c = V_c - (-V_c) = 2V_c$$

$$\frac{V_s(1-k)k}{8LCf^2} = 2V_c = 2kV_s$$

we gives critical value of Cap

$$C_2 = C = \frac{1-k}{16Lf^2} \quad (5.57)$$

\* Single transistor based buck regulator has  $\eta$  greater than 90%  $\rightarrow$  (only single active element) i.e. PFT Top

\* High di/dt is limited by L

\* But i/c current is discontinuous, and a i/c smoothing filter is generally required.  $\rightarrow$  limitation of Buck regulator

\* ~~Pro~~ Protection ckt is required in case of short ckt across diode.

\* One polarity of opp voltage with unidirectional opp current.

5.5 Finding values of LC filter for Buck regulator?

$V_s = 12V$ ,  $V_a = 5V$  (average required)  
 $R = 500\Omega$  and p-p o/p ripple voltage is  $\approx 20mV$ . The frequency is  $25kHz$ . If p-p ripple current is limited to  $\approx 0.8A$ , Determine:

- (a)  $k$
- (b)  $L$
- (c)  $C$  and
- (d) Critical value of  $L \frac{1}{2} C$ .

eg (5.52)

$$\Delta I = \frac{V_a (V_s - V_a)}{f L V_s}$$

(5.49)

$$k = \frac{V_a}{V_s} = \frac{5}{12} = 0.42$$

eg (5.52) gives

$$L = \frac{V_a (V_s - V_a)}{f \Delta I V_s}$$

$$L = \frac{5(12-5)}{(25k)(0.8)12}$$

$$L = 145.8 \mu H$$

eg (5.55)

$$\Delta V_c = \frac{V_s k (1-k)}{8LCf^2} \quad [C = 200 \mu F]$$

$$C = \frac{V_s k (1-k)}{8L \Delta V_c f^2} \Rightarrow C = \frac{12(0.42)(1-0.42)}{8(145.8\mu)(20m)(25k)^2}$$

$$L_c = \frac{(1-k)R}{2f}$$

$$= \frac{(1-0.42)500}{2(25k)}$$

$$L_c = 5.8mH$$

$$C = \frac{1-k}{16Lf^2}$$


$$= \frac{1-0.42}{16(5.8m)(25k)^2}$$

$$C = 10nF$$




(Week: 15)



# BOOST Regulator

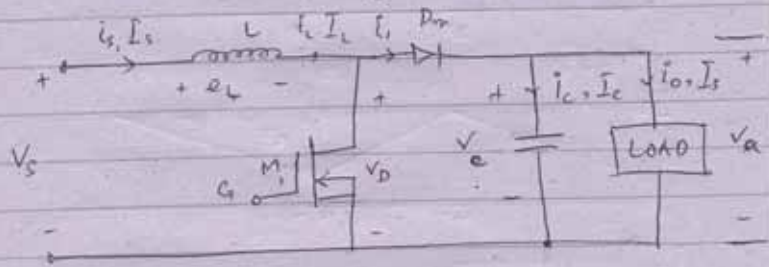

- Inductance is shifted in 1/p
- Switching element is in || with off.
- Diode is shifted after switch so only rve pulse goes on.

 

load is being supplied by capacitor

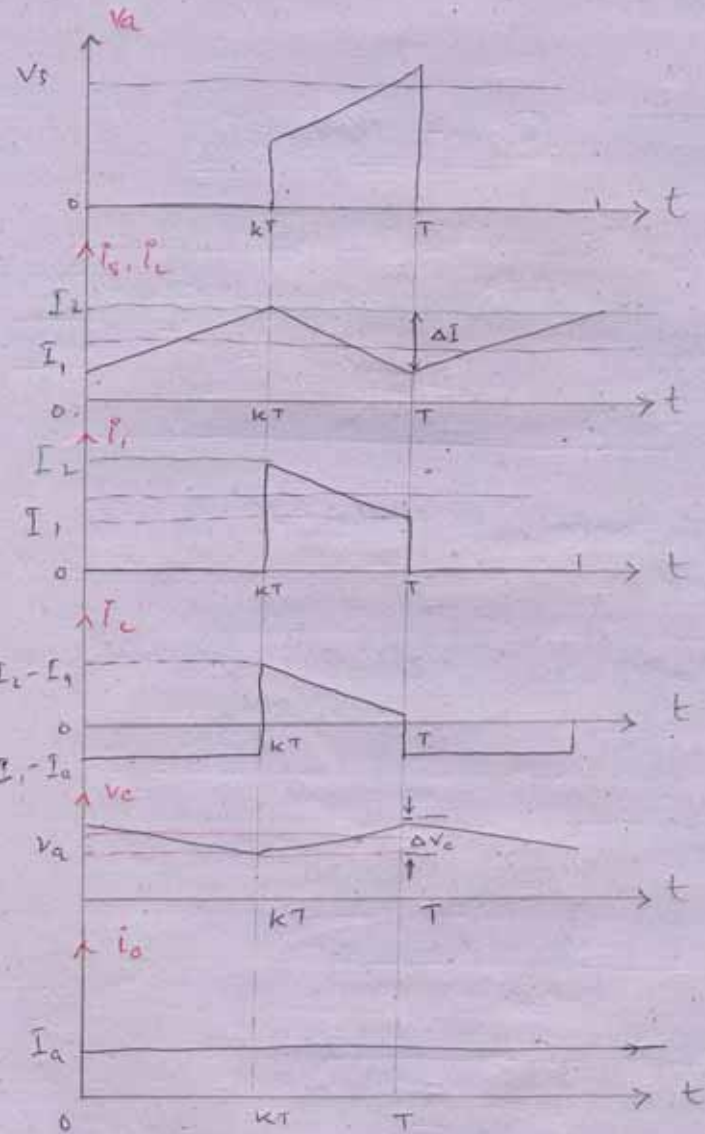 

Diode current

Assuming inductor current rises linearly from  $I_1$  to  $I_2$  in time  $t_1$

$$V_s = L \frac{I_2 - I_1}{t_1} = L \frac{\Delta I}{t_1} \quad (5.58)$$

or

$$t_1 = \frac{\Delta I L}{V_s} \quad (5.59)$$

and inductor current falls from  $I_2$  to  $I_1$  in time  $t_2$

$$V_s - V_a = -L \frac{\Delta I}{t_2} \quad (5.60)$$

or

$$t_2 = \frac{\Delta I L}{V_a - V_s} \quad (5.61)$$

where  $\Delta I = I_2 - I_1$  is peak-peak ripple current of 'L' from eq. (5.58) and (5.60)

$$\Delta I = \frac{V_s t_1}{L} = \frac{(V_a - V_s) t_2}{L}$$

Substituting  $t_1 = kT$  and  $t_2 = (1-k)T$  yields average o/p voltage

$$V_a = V_s \frac{T}{t_1} = \frac{V_s}{1-k} \quad (5.62)$$

we get

$$(1-k) = \frac{V_s}{V_a} \quad (5.63)$$

Substituting  $k = \frac{t_1}{T} = t_1 f$  in (5.63)

$$t_1 = \frac{V_a - V_s}{V_a f} \quad (5.64)$$

Assuming a lossless diode  $V_s I_s = V_a I_a$   
 $V_s I_a / (1-k)$  and avg 'p' current is

$$I_s = \frac{I_a}{1-k} \quad (5.65)$$

The switching period  $T$  can be found

$$T = \frac{1}{f} = t_1 + t_2 = \frac{\Delta I L}{V_s} + \frac{\Delta I L}{V_a - V_s}$$

$$T = \frac{\Delta I L V_a}{V_s (V_a - V_s)} \quad (5.66)$$



(9)

and this gives p-p ripple current

$$\Delta I = \frac{V_s(V_a - V_s)}{f V_a L} \quad (5.67)$$

$$\Delta I = \frac{V_s k}{f L} \quad (5.68)$$

when transistor is on, cap supplies load for  $t = t_1$ . The avg cap current during time  $t_1$  is  $I_c = I_a$  and p-p ripple voltage of cap is

$$\Delta V_c = V_c - V_c(t=0) = \frac{1}{C} \int_0^{t_1} I_c dt = \frac{1}{C} \int_0^{t_1} I_a dt$$

$$\Delta V_c = \frac{I_a t_1}{C} \quad (5.69)$$

Substituting  $t_1 = \frac{(V_a - V_s)}{V_a f}$  from (5.64)

$$\Delta V_c = \frac{I_a (V_a - V_s)}{V_a f C} \quad (5.70)$$

$$\Delta V_c = \frac{I_a k}{f C} \quad (5.71)$$

Condition for continuous current Inductor and Capacitor voltage:

If  $I_L$  is avg L current, inductor ripple current  $\Delta I_L = 2 I_L$ .

Eq (5.62) and (5.68) we get

$$\frac{k V_s}{f L} = 2 I_L = 2 I_a = \frac{2 V_s}{(1-k) R}$$

we gives critical value of L as

$$L_c = L = \frac{k(1-k) R}{2f} \quad (5.72)$$

If  $V_c$  is avg cap voltage capacitor ripple voltage  $\Delta V_c = 2 V_{cr}$  eq (5.71) we get

$$\frac{I_a k}{C f} = 2 V_a = 2 I_a R$$

we give critical value of Cap

$$C_c = C = \frac{k}{2f R} \quad (5.73)$$

(Boost Regulator)

(161)

15-05-08

Circuit properties:

(1)

Boost reg step up voltage without a transformer. High  $\eta$  due to single transistor operation.

Input current is continuous, however a high peak current has to flow thru the trans.  $\rightarrow$  (High PIV rating req)

Output voltage is very sensitive to duty cycle (k).

Stabilization of output voltage can be a problem.

Solution: Use ripple filter at output.

The avg output current is  $<$  average inductor current by a factor  $1-k$ .

Much higher rms current to pass thru filter cap.

Hence larger filter cap and inductor than buck reg are required.

Ex: 5.6  $V_s = 5V$ ,  $V_o = 15V$ ,  $I_o = 0.5A$

$f = 25kHz$ ,  $L = 150\mu H$  and  $C = 220\mu F$   
determine (a) k (b)  $\Delta I$  (c)  $I_2$

(d)  $\Delta V_o$  (e) Critical  $L_c$  &  $C_c$

sol

eq (5.63)

$$k = 1 - \frac{V_o}{V_s}$$

(a)  $k = 1 - 0.667$

eq (5.68)

(b)  $\Delta I = \frac{V_s k}{fL}$

$$= \frac{(5)(0.667)}{(25k)(150\mu H)}$$

$$\Delta I = 0.89 A$$

(c)

eq (5.69)  $I_2 = I_s + \frac{\Delta I}{2}$   
 $I_s = \frac{I_o}{1-k}$   
 $I_2 = \frac{1.5 + 0.89}{2}$

(d)

eq (5.70)  $\Delta V_o = \frac{I_o k}{fC}$   
 $= \frac{(0.5)(0.667)}{(25k)(220\mu F)}$

(162)

$$\Delta V_o = 60.63 mV$$

$$(e) L_c = \frac{k(1-k)R}{2f}$$

$$R = \frac{V_o}{I_o} = \frac{15}{0.1} = 30 \Omega$$


$$L_c = \frac{(0.667)(1-0.667)30}{2(25k)}$$

$$L_c = 133 \mu H$$

$$C_c = \frac{k}{2fR}$$

$$= \frac{0.667}{2(25k)30}$$

$$C_c = 444.6 \mu F$$



 


Q/17 Rework the problem by taking duty cycle = 60%

Q/18 Rework problem when switching freq is altered to 50kHz with k => (1) 66% (2) 60%
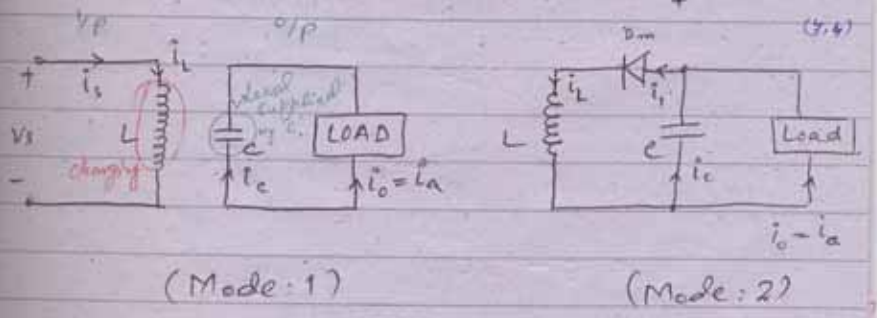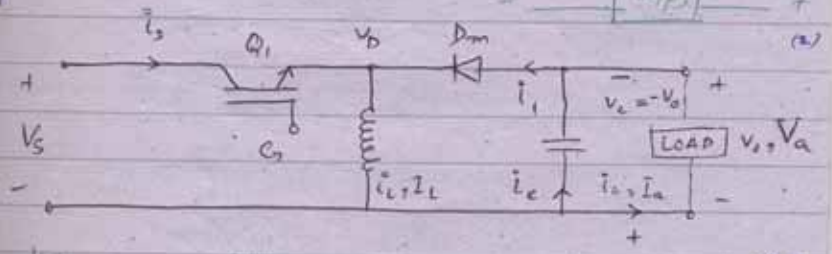 
# Buck-Boost


A buck-boost reg provides an o/p voltage that may be less than or greater than i/p voltage - hence known as "Buck-Boost". o/p voltage polarity is opposite to that of i/p voltage. This reg is also known as an inverting regulator. The ckt arrangement of a buck-boost reg is shown in fig (5-18a)



The ckt operation can be divided into two modes. During mode 1, transistor is turned ON. Diode Dm is reverse biased. The i/p current,  $i_s$  rises, ~~flow~~ flows thru 'L' and  $Q_1$ . During mode 2 trans  $Q_1$  is switched off and current,  $i_c$  was flowing thru L would flow thru L, C, Dm and load. The energy stored in inductor would be transferred to load and the inductor current fall until trans  $Q_1$  is switched ON again in next cycle. The equivalent ckt for modes are shown. The wave forms for steady state voltage and current of B-B reg are shown in (fig 5-18c) for continuous load current.

(Buck-Boost)

(5)

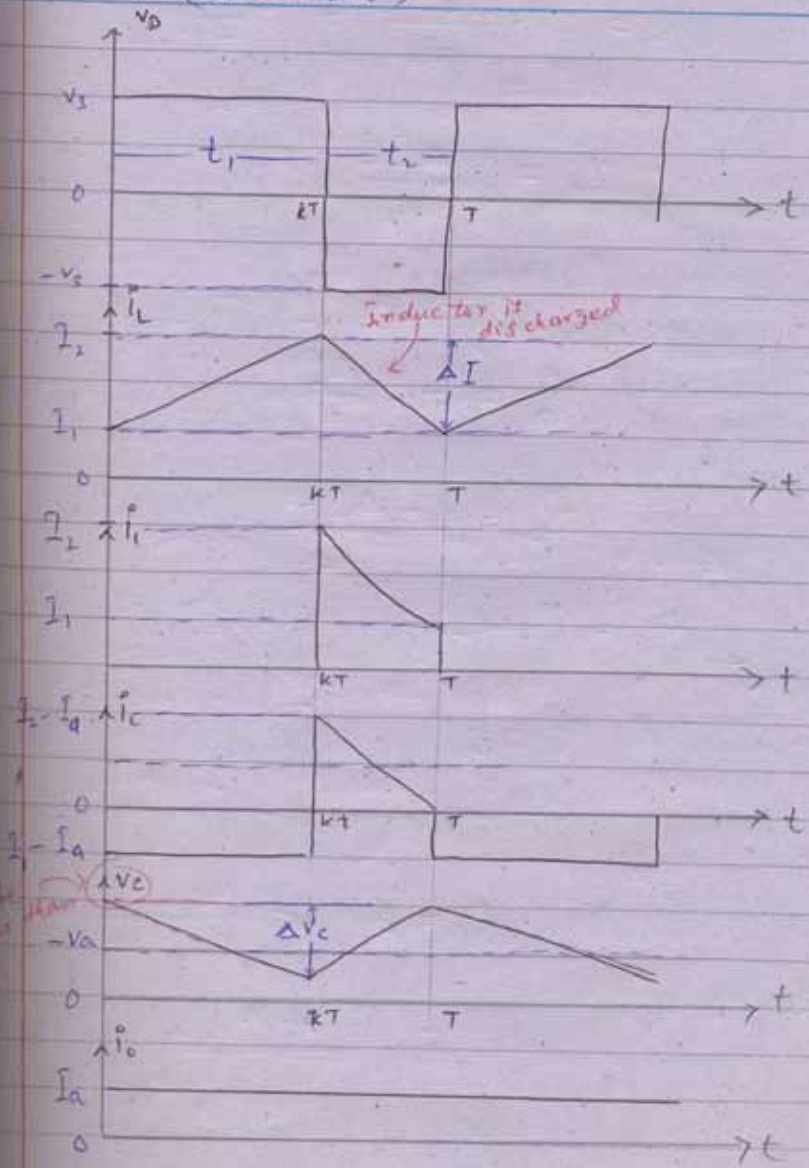

Assuming that inductor current rises linearly from  $I_1$  to  $I_2$  in time  $t_1$ ,

$$V_s = L \frac{I_2 - I_1}{t_1} = L \frac{\Delta I}{t_1} \quad (5.75)$$

or

$$t_1 = \frac{\Delta I L}{V_s} \quad (5.75)$$

$\times$   $I_L$  falls linearly from  $I_2$  to  $I_1$  in  $t_2$

$$V_a = -L \frac{\Delta I}{t_2} \quad (5.76)$$

$$t_2 = \frac{-\Delta I L}{V_a} \quad (5.77)$$

where  $\Delta I = I_2 - I_1$  is p-p ripple current of inductor 'L' from eqs (5.75) and (5.76)

$$\Delta I = \frac{V_s t_1}{L} = \frac{-V_a t_2}{L}$$

Substituting  $t_1 = kT$  and  $t_2 = (1-k)T$  in eq (5.77)  $\Rightarrow$

$$V_a = \frac{V_s k}{1-k} \quad (5.78)$$

(5.78)

(Buck-Boost)

Substituting  $t_1 = kT$  and  $t_2 = (1-k)T$  into eq 5.79

$$t_1 = kT \quad \text{and} \quad t_2 = (1-k)T \quad \text{into} \quad (5.78)$$

$$(1-k) = \frac{-V_s}{V_a - V_s} \quad (5.79)$$

Substituting  $t_2 = (1-k)T$  and  $(1-k)$  from eq (5.79) in eq (5.78) yields

$$t_1 = \frac{V_a}{(V_a - V_s)f} \quad (5.80)$$

Assuming lossless ckt  
 $V_s I_s = -V_a I_a = V_s I_a k$  and  
 avg 'p' current is  $(1-k)$  related  
 to avg op current  $I_a$  by

$$I_s = \frac{I_a k}{1-k} \quad (5.81)$$

The switching period  $T$  can be found from

$$T = \frac{1}{f} = t_1 + t_2 = \frac{\Delta I_L}{V_s} + \frac{\Delta I_L}{V_a - V_s} \quad (5.82)$$

$$T = \frac{V_a \Delta I_L (V_a - V_s)}{V_s V_a}$$

and gives p-p ripple current

$$\Delta I = \frac{V_s k}{fL} \quad (5)$$

or

$$\Delta I =$$

\* when  $Q_1$  is ON, filter cap supplies load current for  $t = t_1$ . The avg discharging current of cap is  $I_c = I_a$  and peak-pk ripple vol of cap is

$$\Delta V_c = \frac{1}{C} \int_0^{t_1} I_c dt = \frac{1}{C} \int_0^{t_1} I_a dt$$

$$\Delta V_c = \frac{I_a t_1}{C} \quad (5.85)$$

Substituting  $t_1 = \frac{V_a}{(V_a - V_s)f}$  from eq (5.80) becomes;

$$\Delta V_c = \frac{I_a V_a}{(V_a - V_s) f C} \quad (5)$$

or

$$\Delta V_c = \frac{I_a k}{f C} \quad (5)$$

Condition for Continuous inductor current &

Capacitor voltage:

If  $I_L$  is avg inductor current, inductor ripple  $\Delta I_L = 2I_L$  using eq (5.78)  
& (5.84) we get

$$\frac{kV_s}{fL} = 2I_L = 2I_a = \frac{2kV_s}{(1-k)R}$$

we give critical value of  $L_c$

$$L_c = L = \frac{(1-k)R}{2f} \quad (5.88)$$

If  $V_c$  is avg cap voltage, capacitor ripple voltage  $\Delta V_c = 2V_a$  using eq (5.87) we get

$$\frac{I_a k}{Cf} = 2V_a = 2I_a R$$

we give critical value of  $C$

$$C_c = C = \frac{k}{2fR} \quad (5.89)$$

(15)  
+

\* A B-B reg provides o/p voltage polarity reversal without txfr

\* It has high  $\eta$ .

\* Under fault condition of tran h  $di/dt$  is limited by inductor

\* o/p short ckt protection is easy to implement.

\*  $I_p$  current is discontinuous & a high peak current flows thru tran Q.

Ex 5.7:  $V_s = 12V$ ,  $k = 0.25$ ,  $f = 25kHz$

$L = 1750\mu H$ ,  $C = 220\mu F$ ,  $I_a = 1.25A$ .

Determine (a)  $V_a$  (b)  $\Delta V_c$  (c)  $\Delta I$

$I_p$  (d) Critical  $L$  and  $C$ ?

$$\Delta V_c = \frac{I_a t_1}{C} \quad (5.85)$$

$$t_1 = \frac{V_a}{V_s - V_a} \quad V_a = \frac{V_s k}{1-k} \quad (5.86)$$

$$t_1 = \frac{V_a V_s}{(V_s - V_s) f}$$

$$\begin{aligned}
 (a) \quad V_a &= \frac{V_s k}{(1-k) f} \\
 &= \frac{(12)(0.25)}{(1-0.25) 25k} \\
 V_a &= 4
 \end{aligned}$$

$$\begin{aligned}
 (b) \quad \Delta V_c &= \frac{I_a t_1}{C} && \text{eq (5.87)} \\
 t_1 &= \frac{V_a}{(V_a - V_s) f} && \Delta V_c = \frac{I_a k}{f C} \\
 &= \frac{4}{(4-12) 25k} && \Delta V_c = 56.8 \text{ mV} \\
 t_1 &= 20 \mu\text{s} \\
 \Delta V_c &= \frac{(1.25)(20 \mu\text{s})}{220 \mu\text{s}} \\
 \Delta V_c &= -0.125 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 (c) \quad \Delta I &= \frac{V_s \cdot k}{f L} \\
 &= \frac{(12)(0.25)}{(25k)(150 \mu\text{s})} \\
 \Delta I &= 0.8 \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 (e) \quad L_c &= \frac{(1-k) R}{2f} && R = \frac{V_a}{I_c} = \\
 L_c &> \frac{(1-0.25) 3.2}{2(25k)} \\
 L_c &= 48 \mu\text{H}
 \end{aligned}$$

$$\begin{aligned}
 C &= \frac{k}{2fR} \\
 &= \frac{0.25}{2(25k) 3.2} \\
 C &= 1.56 \mu\text{F}
 \end{aligned}$$

$$\begin{aligned}
 (d) \quad I_s &= \frac{1.25 \times 0.25}{(1-0.25)} = 0.4167 \text{ A} \\
 I_p &= \frac{I_s}{k} + \frac{\Delta I}{2} \\
 &= \frac{0.4167}{0.25} + \frac{0.8}{2} \\
 I_p &= 2.067 \text{ A}
 \end{aligned}$$



# MOTOR DRIVES

## (Introduction to Solid State Drives)

- \* In industrial application electrical motors are extensively used. (21)
- \* Both DC and AC motor are utilized in industry.
- \* Motor drives are electrical electronic ckt's that can control speed & subsequently torque of these motors.
- \* Two types of drives:

(i) DC Drives      (ii) AC Drives


- \* DC motors have variable characteristics and are extensively used in industry.
- \* They can provide high starting torque and their speed can be controlled over a wide range.
- \* The methods of speed control are usually simpler and less expensive than AC motors.

- \* Both series and separately excited (dc) are used in variable speed drive.
- \* Usually series motors are preferred for traction applications.
- \* Due to commutators, dc motors are not recommended for high speed applications.
- \* DC motors require more maintenance as compared to ac motors.
- \* Modern advancements in power electronics have enabled ac motor drives to become more competitive with dc drives.
- \* Future belongs to ac drives but currently dc drives are mostly employed.
- \* It might be a few decades more when dc drives will fully be replaced by ac drives.
- \* Controlled rectifiers can generate a variable dc opp from ac I/p

\* A dc to dc converter can generate a variable dc off from a fixed dc i/p.

\* The controlled rectifier and dc to dc converters have revolutionized dc drives concept and now variable speed dc drives have power levels from fractional horsepower to several megawatts.

 
\* Controlled rectifier are generally used for speed control of dc motor as shown below:



Controlled rectifier

Bridge or controlled rect

{ (a) Controlled rect-fed drives }

 

Bridge rect DC-DC Conv Bridge cont rect

{ (b) Chopper fed drive }

\* Speed of a dc motor can be varied by controlling (1) Armature voltage (2) Field current (3) Armature current that is a measure of torque demand.

\* For a speed less than rated speed (also known as base speed) the arm voltage is varied to control speed while arm and field currents maintained constant. For a speed higher than rated speed, field current is varied to control speed while arm voltage is maintained at rated value.

\* DC drives can be classified, into 3 types:

- o Single  $\phi$
- o 3  $\phi$
- o DC-DC converter drives.

AC motors are light weight (20 to 40% lesser than dc motor).

In expensive

low maintainance.

For variable speed they require freq and voltage & current.

Power converter, inverter & ac controllers can control freq, voltage & current to meet drive requiremets. (25)

Two type of AC drives:

- Induction motor Drives
- Synchronous " "

Methods:

- stator voltage control.
- rotor " "
- Proqruency control. (30)

